

# ECE 2300 Digital Logic and Computer Organization Fall 2024

## Topic 1: Digital Circuits

School of Electrical and Computer Engineering  
Cornell University

revision: 2024-08-29-04-05


<b>1</b>	<b>Analog View of a Transistor</b>	<b>3</b>
<b>2</b>	<b>Digital View of a Transistor</b>	<b>5</b>
	2.1. Binary Digital Abstraction . . . . .	5
	2.2. Switch-Level Model for a Transistor . . . . .	6
	2.3. Transistor Networks . . . . .	8
<b>3</b>	<b>CMOS Inverter</b>	<b>10</b>
<b>4</b>	<b>Simple Digital CMOS Circuits</b>	<b>12</b>
	4.1. Rules for Digital CMOS Circuits . . . . .	15
<b>5</b>	<b>More Complex Digital CMOS Circuits</b>	<b>16</b>
	5.1. Multi-Input Digital Circuits . . . . .	16
	5.2. Multi-Stage Digital Circuits . . . . .	18
<b>6</b>	<b>Summary of Abstractions</b>	<b>19</b>

---


Copyright © 2024 Christopher Batten. All rights reserved. This handout was prepared by Prof. Christopher Batten at Cornell University for ECE 2300 / ENGRD 2300 Digital Logic and Computer Organization. Download and use of this handout is permitted for individual educational non-commercial purposes only. Redistribution either in part or in whole via both commercial or non-commercial means requires written permission.
 
# 1. Analog View of a Transistor


- **Transistors:** Invented by John Bardeen, Walter Brattain, and William Shockley at Bell Labs in 1947
- **Integrated Circuits:** Independently developed by Jack Kilby (at TI) and Robert Noyce (at Fairchild) in the 1950s; Noyce and Gordon Moore founded Intel in 1968



 
- **Intel Sapphire Rapids (2023)**
  - Number of transistors: 61 billion
  - Technology node: Intel 7


 
## Metal-Oxide Semiconductor Field-Effect Transistor (MOSFET)




 - MOS: Need three materials to make a transistor
  - \_\_\_\_\_ strong conductor of current
  - \_\_\_\_\_ insulator (does not conduct)
  - \_\_\_\_\_ conduction can be controlled
- FET: Electric field causes conduction between source and drain





- MOSFET operation
  - As gate voltage increases, current from drain to source also increases
  - At specific threshold voltage, current starts to increase very rapidly
- MOSFET analog applications
  - Various amplifiers
  - Operational amplifiers
  - Current sources and mirrors
  - Voltage-controlled oscillators
  - Voltage regulators
  - Filters

## 2. Digital View of a Transistor


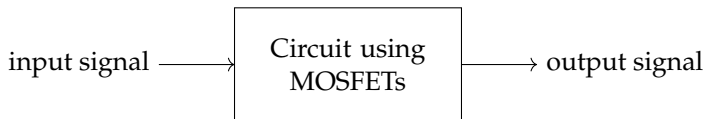

  
### 2.1. Binary Digital Abstraction



Analog circuits (continuous values are possible)



  Binary digital circuits (only two specific values are possible)





  Abstract low voltage as "logic 0" and high voltage as "logic 1"



  
## 2.2. Switch-Level Model for a Transistor

- Non-linear change in current make transistors act like switches
  - If  $g = 0$ , then the switch is open
  - If  $g = 1$ , then the switch is closed



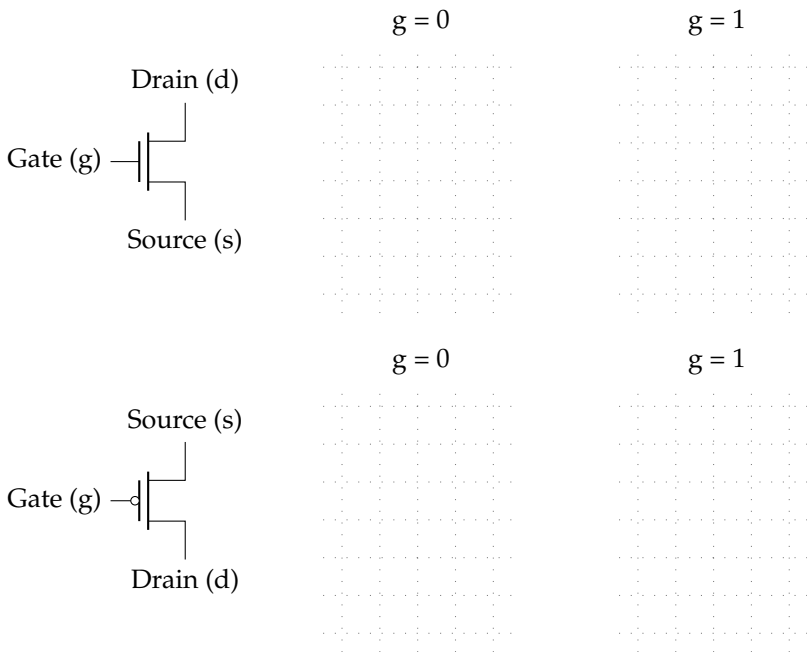
- Two different kinds of MOSFETs
  - **NMOS**: Closed when  $g = 1$ , open when  $g = 0$ , better at passing 0
  - **PMOS**: Closed when  $g = 0$ , open when  $g = 1$ , better at passing 1



 
- NMOS and PMOS have complementary properties
  - For same input, one will be on and one will be off
  - Digital CMOS circuits combine NMOS and PMOS transistors









$a = 0 \quad b = 0$

 



$a = 0 \quad b = 1$

 

$a = 1 \quad b = 0$

 

$a = 1 \quad b = 1$

  

$a = 0 \quad b = 0$



$a = 0 \quad b = 1$




$a = 1 \quad b = 0$



$a = 1 \quad b = 1$



### 3. CMOS Inverter

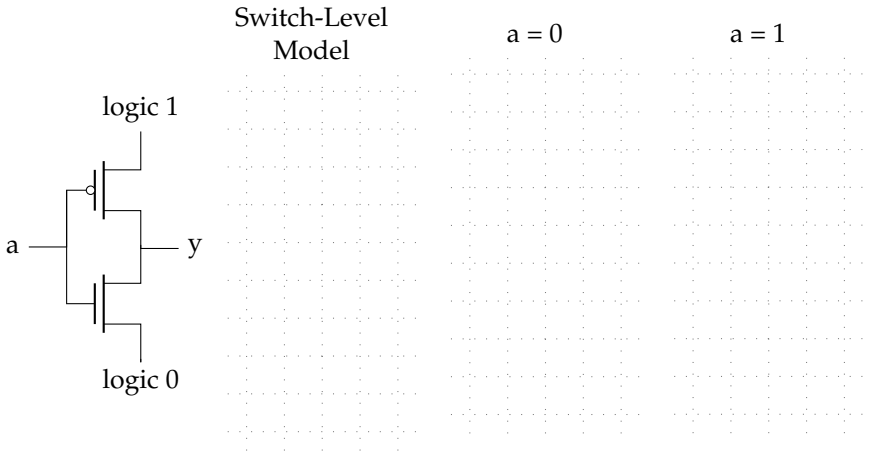


#### Truth Table

- Rows for all possible input values
- Specifies output for to given input values


a	y
 
#### Waveform

- Illustrates how outputs change over time for given input signals
- Various delay models are possible



## Switch-Level Modeling in Verilog

 

```

1  module Inverter
2  (
3      output y,
4      input a
5  );
6
7      supply1 vdd;
8      supply0 gnd;
9
10     pmos p0( y, vdd, a );
11     nmos n0( y, gnd, a );
12
13 endmodule


```

- supply1 is used to create a “logic 1” power supply
- supply0 is used to create a “logic 0” ground
- pmos( drain, source, gate ) instantiates a PMOS transistor
- nmos( drain, source, gate ) instantiates a PMOS transistor
- module/endmodule used to define a hardware module along with the corresponding input and output ports


<https://www.edaplayground.com/x/LbpL>

## 4. Simple Digital CMOS Circuits

Transistor-Level Schematic

 


Switch-Level Model

 

Truth Table


a	b	y

Waveform

 


<https://www.edaplayground.com/x/wHkB>

Transistor-Level Schematic

 


Switch-Level Model

 


Truth Table

a	b	y


Waveform

 

Transistor-Level Schematic

 


Switch-Level Model

 

Truth Table


a	b	y

Waveform

 
 
## 4.1. Rules for Digital CMOS Circuits

- Use NMOS and PMOS transistors such that:
  - There should never be a direct path from Vdd to ground
  - The output should never be floating
- Circuit is divided into two parts:
  - Pull-up network exclusively uses PMOS transistors
  - Pull-down network exclusively uses NMOS transistors
- The pull-up and pull-down networks are duals of each other
  - Two transistors in series in the pull-down network will be in parallel in the pull-up network
  - Two transistors in parallel in the pull-down network will be in series in the pull-up network
  - Apply these rules hierarchically to subnets
- There should always be an equal number of PMOS and NMOS transistors




## 5. More Complex Digital CMOS Circuits

### 5.1. Multi-Input Digital Circuits





a	b	c	y

 



  
Finish the circuit using the rules for digital CMOS circuits, then fill in the truth table.




a	b	c	y

## 5.2. Multi-Stage Digital Circuits

Transistor-Level Schematic

 


Switch-Level Model

 



Truth Table

a	b	x	y

Waveform

 

## 6. Summary of Abstractions

  

a	y
0	1
1	0