


# ECE 2300 Digital Logic and Computer Organization Fall 2024

## Topic 3: Boolean Equations

School of Electrical and Computer Engineering  
Cornell University

revision: 2024-09-10-10-35


<b>1</b>	<b>From Logic Gates to Boolean Equations</b>	<b>3</b>
1.1.	Writing Boolean Equations in Verilog . . . . .	5
<b>2</b>	<b>From Truth Tables to Boolean Equations</b>	<b>6</b>
2.1.	Sum-of-Products Canonical Form . . . . .	6
2.2.	Product-of-Sums Canonical Form . . . . .	7
2.3.	Using Canonical Forms in Verilog . . . . .	8
<b>3</b>	<b>Boolean Algebra</b>	<b>10</b>
3.1.	Boolean Axioms, Theorems, and Proofs . . . . .	10
3.2.	Simplifying with Boolean Algebra . . . . .	13
3.3.	Simplifying with Karnaugh Maps . . . . .	15
<b>4</b>	<b>From Boolean Equations to Logic Gates</b>	<b>18</b>
<b>5</b>	<b>From Boolean Equations to Transistor Schematics</b>	<b>21</b>
<b>6</b>	<b>Summary of Abstractions</b>	<b>22</b>

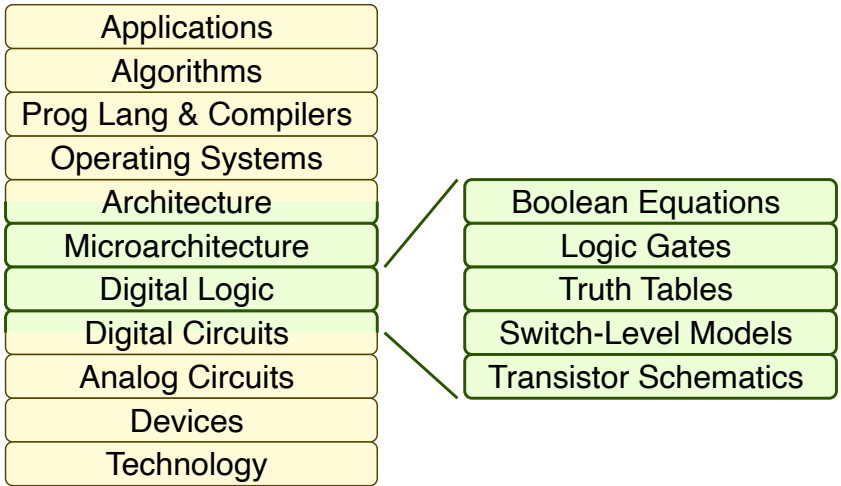


Copyright © 2024 Christopher Batten. All rights reserved. This handout was prepared by Prof. Christopher Batten at Cornell University for ECE 2300 / ENGRD 2300 Digital Logic and Computer Organization. Download and use of this handout is permitted for individual educational non-commercial purposes only. Redistribution either in part or in whole via both commercial or non-commercial means requires written permission.
 
## 1. From Logic Gates to Boolean Equations


- Start by defining some terminology
  - \_\_\_\_\_ : equation where all variables are TRUE or FALSE
  - \_\_\_\_\_ : variable or its inverse (complement of  $A$  is  $\bar{A}$ )
  - \_\_\_\_\_ : variable or its complement ( $A, B, \bar{A}, \bar{B}$ )
  - \_\_\_\_\_ : AND of one or more literals ( $\bar{A}B, A\bar{B}C, B$ )
  - \_\_\_\_\_ : another name for a product
  - \_\_\_\_\_ : product involving all inputs to function ( $A\bar{B}C$ )
  - \_\_\_\_\_ : OR of one or more literals ( $A + \bar{B}, B$ )
  - \_\_\_\_\_ : sum involving all inputs to function ( $A + \bar{B} + C$ )
- We can represent our primitive logic gates as Boolean equations
  - Higher level of abstraction makes it easier to understand, manipulate, and optimize gate-level networks




$$Y = \bar{A}$$

 


$$Y = AB$$

 


$$Y = \overline{AB}$$

 


$$Y = A + B$$

 


$$Y = \overline{A + B}$$

 


$$Y = A \oplus B$$

 

$$Y = \overline{A \oplus B}$$

 

Corresponding Boolean equation

 

Corresponding Boolean equation



## 1.1. Writing Boolean Equations in Verilog

NOT	$Y = \overline{A}$	<code>assign Y = ~A;</code>
AND	$Y = AB$	<code>assign Y = A &amp; B;</code>
NAND	$Y = \overline{AB}$	<code>assign Y = ~(A &amp; B);</code>
OR	$Y = A + B$	<code>assign Y = A   B;</code>
NOR	$Y = \overline{A + B}$	<code>assign Y = ~(A   B);</code>
XOR	$Y = A \oplus B$	<code>assign Y = A ^ B;</code>
XNOR	$Y = \overline{A \oplus B}$	<code>assign Y = ~(A ^ B);</code>

$$W = \overline{A}$$

$$Z = \overline{W}$$

$$X = \overline{C}$$

$$Y = \overline{Z + X}$$

```

1 module BooleanEqEx1
2 (
3     input wire a,
4     input wire b,
5     input wire c,
6     output wire y
7 );
8
9     wire w;
10    wire x;
11    wire z;
12
13    assign w = ~a;
14    assign z = ~( w & b );
15    assign x = ~c;
16    assign y = ~( z | x );
17
18    // assign y = ~( ~( ~a & b ) | ~c )
19
20 endmodule

```



## 2.2. Product-of-Sums Canonical Form

- We can write a Boolean equation for any truth table as the AND of the maxterms for which the output is FALSE minterms for which the output is TRUE
- Called product-of-sums (POS) canonical form

$A$	$B$	$Y$	maxterm	name
0	1	1	$A + B$	$M_0$
0	1	0	$A + \bar{B}$	$M_1$
1	0	1	$\bar{A} + B$	$M_2$
1	1	1	$\bar{A} + \bar{B}$	$M_3$

Corresponding Boolean equation



$A$	$B$	$Y$	maxterm	name
0	1	0	$A + B$	$M_0$
0	1	1	$A + \bar{B}$	$M_1$
1	0	0	$\bar{A} + B$	$M_2$
1	1	1	$\bar{A} + \bar{B}$	$M_3$

Corresponding Boolean equation



## 2.3. Using Canonical Forms in Verilog

- Let's revisit a truth table from the previous topic
- Create a wire for every minterm
- Assign output as the OR of every minterm for which output is TRUE

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

```


1 module SumOfProductsEx
2 (
3   input wire a,
4   input wire b,
5   input wire c,
6   output wire y
7 );
8
9   assign min0 = ~a & ~b & ~c;
10  assign min1 = ~a & ~b & c;
11  assign min2 = ~a & b & ~c;
12  assign min3 = ~a & b & c;
13
14  assign min4 = a & ~b & ~c;
15  assign min5 = a & ~b & c;
16  assign min6 = a & b & ~c;
17  assign min7 = a & b & c;
18
19  assign y = min3 | min4 | min6 | min7;
20
21 endmodule

```

Corresponding Boolean equation





 

### 3. Boolean Algebra

- Algebra enables logically manipulating mathematical equations
- Boolean algebra enables logically manipulating Boolean equations

#### 3.1. Boolean Axioms, Theorems, and Proofs

- The five axioms of Boolean algebra and their duals define Boolean variables and meaning of NOT, AND, OR

Number	Axiom	Dual	Name
A1	$B = 0$ if $B \neq 1$	$B = 1$ if $B \neq 0$	Binary Field
A2	$\overline{0} = 1$	$\overline{1} = 0$	NOT
A3	$0 \cdot 0 = 0$	$1 + 1 = 1$	AND/OR
A4	$1 \cdot 1 = 1$	$0 + 0 = 0$	AND/OR
A5	$0 \cdot 1 = 1 \cdot 0 = 0$	$1 + 0 = 0 + 1 = 1$	AND/OR

- Following theorems describe how to simplify equations involving one variable

Number	Theorem	Dual	Name
T1	$B \cdot 1 = B$	$B + 0 = B$	Identity
T2	$B \cdot 0 = 0$	$B + 1 = 1$	Null Element
T3	$B \cdot B = B$	$B + B = B$	Idempotency
T4	$\overline{\overline{B}} = B$		Involution
T5	$B \cdot \overline{B} = 0$	$B + \overline{B} = 1$	Complements

- Following theorems describe how to simplify equations involving more than one variable

#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B+C = C+B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B+C) (B+D)$	Distributivity
T9	$B \bullet (B+C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	$(B+C) \bullet (B+\bar{C}) = B$	Combining
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	$(B+C) \bullet (\bar{B}+D) \bullet (C+D) = (B+C) \bullet (\bar{B}+D)$	Consensus
T12	$\overline{B \bullet C \bullet D \dots} = \bar{B} + \bar{C} + \bar{D} \dots$	$\overline{B+C+D \dots} = \bar{B} \bullet \bar{C} \bullet \bar{D} \dots$	De Morgan's

- Two methods to prove a theorem
  - Method 1: Perfect induction
  - Method 2: Use other theorems and axioms to make one side of the equation look like the other

$$T9: B \bullet (B + C) = B$$





$$T10: (B \bullet C) + (B \bullet \bar{C}) = B$$



### De Morgan's Theorem

$$T12: \overline{B_0 \bullet B_1 \bullet B_2 \dots} = \bar{B}_0 + \bar{B}_1 + \bar{B}_2 \dots$$



#### NAND

  

$$Y = \overline{AB} = \bar{A} + \bar{B}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

#### NOR

  


$$Y = \overline{A+B} = \bar{A} \bar{B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0
 
### Derive Product-of-Sum from Sum-of-Product

$$Y = \overline{A}\overline{B} + \overline{A}B$$



### 3.2. Simplifying with Boolean Algebra

$$Y = \overline{A}B + AB$$

$$Y = B \quad \text{T10: Combining}$$

$$Y = \overline{A}B + AB$$

$$Y = B(A + \overline{A}) \quad \text{T8: Distributivity}$$

$$Y = B(1) \quad \text{T5': Complements}$$

$$Y = B \quad \text{T1: Identity}$$

$$Y = \overline{A}B\overline{C} + \overline{A}BC + ABC$$

Attempt #1



Attempt #2



### 3.3. Simplifying with Karnaugh Maps

- K-maps are a systematic way to simplify Boolean equations

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$Y = \overline{A}B\overline{C} + \overline{A}BC + ABC$$

		AB			
		00	01	11	10
C	0				
	1				

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$Y = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C}$$

		AB			
		00	01	11	10
C	0				
	1				

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$$Y = \overline{A}\overline{B}\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + A\overline{B}C + ABC$$

		AB			
		00	01	11	10
C	0				
	1				

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Y = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + A\overline{B}\overline{C} + A\overline{B}C + ABC$$

		AB			
		00	01	11	10
C	0				
	1				



- Extending k-maps to equations of four variables


A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$$\begin{aligned}
 Y &= \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD \\
 &+ \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}BC\overline{D} \\
 &+ \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}C\overline{D} + A\overline{B}CD \\
 &+ AB\overline{C}\overline{D} + AB\overline{C}D + ABC\overline{D}
 \end{aligned}$$


		AB			
		00	01	11	10
CD	00				
	01				
	11				
	10				

## 4. From Boolean Equations to Logic Gates

$$Y = \overline{B}C + A\overline{B}$$

 

 
$$Y = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}C$$




$$Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

XOR3

 


$$Y = A \oplus B \oplus C$$

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

 
## Bubble pushing


$$Y = \overline{\overline{\overline{(A+B)C}}D}$$



 
$$Y = \overline{\overline{\overline{(A+B)C}} + \overline{D}}$$



$$Y = \overline{(A+B)C} + \overline{D}$$

 
 
$$Y = \overline{A} \overline{B} C + \overline{D}$$



## 5. From Boolean Equations to Transistor Schematics

$$Y = \overline{(A + B)C}$$



$$Y = \overline{AB + CD}$$



## 6. Summary of Abstractions

