

# ECE 2300 Digital Logic and Computer Organization Fall 2024

## Topic 4: Combinational Building Blocks

School of Electrical and Computer Engineering  
Cornell University

revision: 2024-09-24-09-04

<b>1</b>	<b>Encoders and Decoders</b>	<b>3</b>
1.1.	Encoders . . . . .	3
1.2.	Decoders . . . . .	4
<b>2</b>	<b>Priority Encoders</b>	<b>5</b>
<b>3</b>	<b>Multiplexors and Demultiplexors</b>	<b>7</b>
3.1.	Multiplexors . . . . .	7
3.2.	Demultiplexors . . . . .	9
<b>4</b>	<b>Shifters and Rotators</b>	<b>9</b>
4.1.	Shifters . . . . .	10
4.2.	Rotators . . . . .	12
<b>5</b>	<b>Comparators</b>	<b>13</b>
5.1.	Equality Comparator . . . . .	13
5.2.	Greater-Than Comparator . . . . .	14

---


<b>6</b>	<b>Adders and Subtractors</b>	<b>16</b>
6.1.	Half and Full Adders . . . . .	16
6.2.	Ripple-Carry Adders . . . . .	19
6.3.	Carry-Select Adders . . . . .	20
6.4.	Carry-Lookahead Adders . . . . .	22
6.5.	Subtractors . . . . .	24
6.6.	Half and Full Subtractors . . . . .	24
6.7.	Ripple-Carry Subtractor . . . . .	26
<b>7</b>	<b>Multipliers</b>	<b>27</b>
7.1.	1x1b Multiplier . . . . .	27
7.2.	1x4b Multiplier . . . . .	27
7.3.	4x4b Multiplier . . . . .	28

Copyright © 2024 Christopher Batten. All rights reserved. This handout was prepared by Prof. Christopher Batten at Cornell University for ECE 2300 / ENGRD 2300 Digital Logic and Computer Organization. Download and use of this handout is permitted for individual educational non-commercial purposes only. Redistribution either in part or in whole via both commercial or non-commercial means requires written permission.

## 1. Encoders and Decoders


- *Binary encoder* has  $2^N$  inputs and  $N$  outputs; sets the output value to reflect which input is one assuming exactly one input is one (encodes a one-value as a binary value)
- *Binary decoder* has  $N$  inputs and  $2^N$  outputs and asserts exactly one output depending on the input value (decodes a binary value into a one-hot value)

### 1.1. Encoders

 


$A_3$	$A_2$	$A_1$	$A_0$	$Y_1$	$Y_0$
0	0	0	1		
0	0	1	0		
0	1	0	0		
1	0	0	0		


CD	AB			
	00	01	11	10
00				
01				
11				
10				

 

## 1.2. Decoders

 


$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0				
0	1				
1	0				
1	1				

 

 
## 2. Priority Encoders

- *Priority encoder* indicates the first input that is one (i.e., the highest priority input) using a one-hot output





$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	0	1
0	1	0	0	0	1	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	0	1
1	0	0	0	1	0	0	0
1	0	0	1	0	0	0	1
1	0	1	0	0	0	1	0
1	0	1	1	0	0	0	1
1	1	0	0	0	1	0	0
1	1	0	1	0	0	0	1
1	1	1	0	0	0	1	0
1	1	1	1	0	0	0	1

 - We can leverage abstraction to manage complexity




$A$	$D_{in}$	$Y$	$D_{out}$
0	0		
0	1		
1	0		
1	1		

  

### 3. Multiplexors and Demultiplexors


- *Multiplexor* chooses among several possible inputs based on the value of a *select* signal
- *Demultiplexor* “routes” an input to one of many several possible outputs based on a *select* signal



#### 3.1. Multiplexors

 

$S$	$D_1$	$D_0$	$Y$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


$C$	$AB$	00	01	11	10
0					
1					

 

  



### 3.2. Demultiplexors

 


$S$	$D$	$Y_0$	$Y_1$
0	0		
0	1		
1	0		
1	1		



## 4. Shifters and Rotators

- *Shifter* shifts the input value either left or right by a variable amount specified with a *shift amount* signal; zeros are shifted in
- *Rotator* rotates the input value either left or right by a variable amount specified with a *rotate amount* signal


## 4.1. Shifters

 


S	A <sub>1</sub>	A <sub>0</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

  


S	A <sub>1</sub>	A <sub>0</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 

 


## 4.2. Rotators

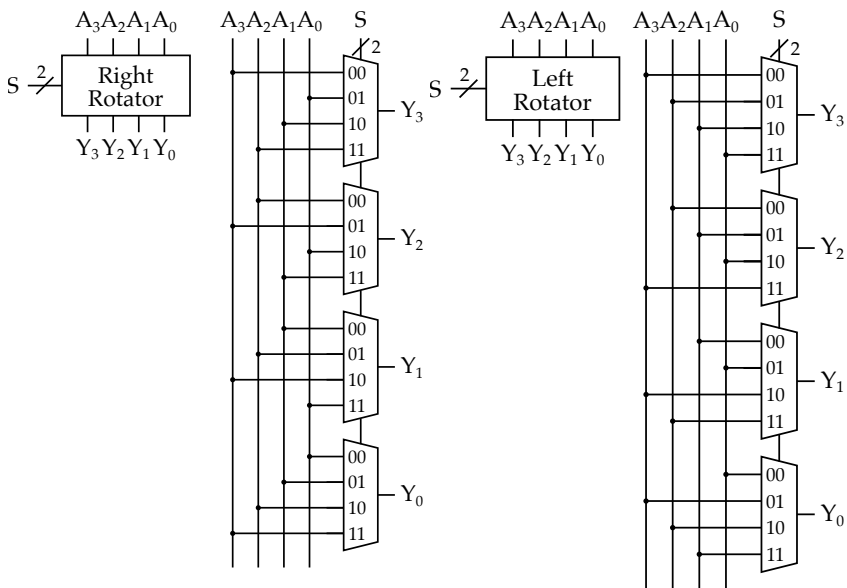


## 5. Comparators

- *Comparator* compares two binary numbers and outputs whether these numbers are equal, if one is greater than the other, or if one is less than the other.

### 5.1. Equality Comparator

 


$A$	$B$	$Y$
0	0	0
0	1	1
1	0	0
1	1	1

 


Gate	$t_{pd}$	$t_{cd}$
AND2	$3\tau$	$3\tau$
XNOR2	$7\tau$	$7\tau$


## 5.2. Greater-Than Comparator

 

0010 (2)	0101 (5)	0111 (7)
0001 (1)	0110 (6)	0101 (5)
$Y =$	$Y =$	$Y =$
1010 (10)	1110 (14)	1010 (10)
1101 (13)	1011 (11)	1010 (10)
$Y =$	$Y =$	$Y =$

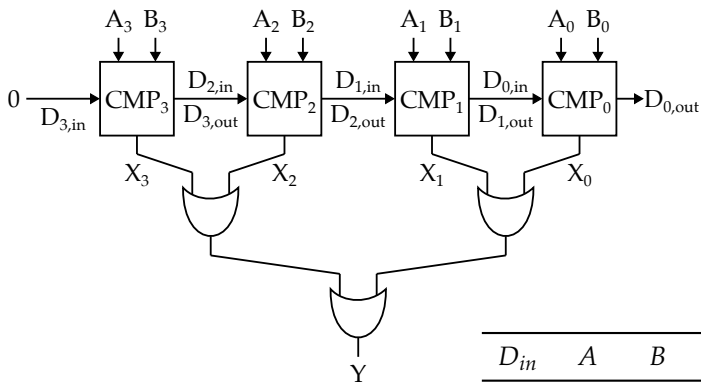

$D_{in}$	$A$	$B$	$X$	$D_{out}$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 

Gate	$t_{pd}$	$t_{cd}$
NOT	$1\tau$	$1\tau$
AND2	$3\tau$	$3\tau$
OR2	$4\tau$	$4\tau$
XOR2	$7\tau$	$7\tau$

Path	Propagation Delay
$A \rightarrow X$	
$B \rightarrow X$	
$D_{in} \rightarrow X$	
$A \rightarrow D_{out}$	
$B \rightarrow D_{out}$	
$D_{in} \rightarrow D_{out}$	


## 6. Adders and Subtractors

- We will gradually build up complexity to explore a variety of different adder designs

$$\begin{array}{r}
 0001 \\
 + 0001 \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0010 \\
 + 0010 \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0010 \\
 + 0010 \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0010 \\
 + 0010 \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0110 \\
 + 0011 \\
 \hline
 \end{array}$$

### 6.1. Half and Full Adders


- Half adder* adds two one-bit numbers

 

A	B	C <sub>out</sub>	S
0	0		
0	1		
1	0		
1	1		



 - *Full adder* adds three one-bit numbers




$A$	$B$	$C_{in}$	$C_{out}$	$S$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

<b>Gate</b>	$t_{pd}$	$t_{cd}$
NOT	$1\tau$	$1\tau$
AND2	$3\tau$	$3\tau$
OR2	$4\tau$	$4\tau$
XOR2	$7\tau$	$7\tau$

<b>Path</b>	<b>Propagation Delay</b>
$A \rightarrow S$	
$B \rightarrow S$	
$C_{in} \rightarrow S$	
$A \rightarrow C_{out}$	
$B \rightarrow C_{out}$	
$C_{in} \rightarrow C_{out}$	
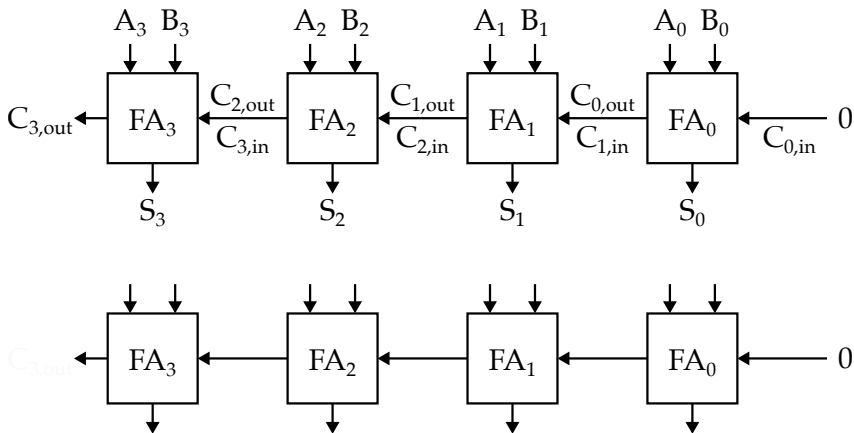
## 6.2. Ripple-Carry Adders



- *Ripple-carry adder* chains full adders together




Path	Propagation Delay
$A_0 \rightarrow S_3$	
$B_0 \rightarrow S_3$	
$A_0 \rightarrow C_{3,out}$	
$B_0 \rightarrow C_{3,out}$	
 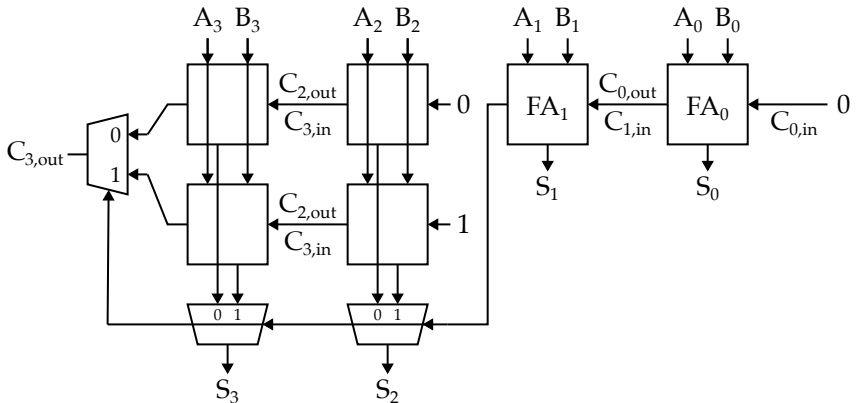
### 6.3. Carry-Select Adders

- Carry-select adder computes most-significant bits twice: once assuming middle of carry chain is zero, once assuming middle of carry chain is one; then selects correct output once middle of carry chain is known



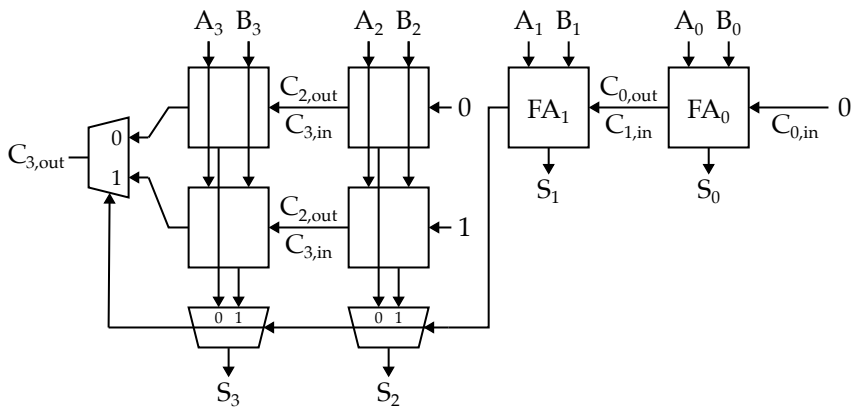

Mux Propagation  
Path Delays

Path	Propagation Delay
$S \rightarrow Y$	$10\tau$
$D_0 \rightarrow Y$	$9\tau$
$D_1 \rightarrow Y$	$9\tau$

Propagation  
Delay

Path	Propagation Delay
$A_0 \rightarrow S_3$	
$B_0 \rightarrow S_3$	
$A_0 \rightarrow C_{3,out}$	
$B_0 \rightarrow C_{3,out}$	

## 6.4. Carry-Lookahead Adders


- *Carry-lookahead adder* computes a *generate* and *propagate* signal for blocks of bits in parallel; then quickly computes the carry signal for every block before finally computing the sum in parallel
- Bit-slice  $i$  *generates* a carry if it produces a carry output independent of the carry input ( $G_i = A_i B_i$ )
- Bit-slice  $i$  *propagates* a carry if it produces a carry output whenever there is a carry input ( $P_i = A_i + B_i$ )

$$\begin{aligned} C_i &= A_i B_i + A_i C_{i-1} + B_i C_{i-1} \\ &= A_i B_i + (A_i + B_i) C_{i-1} \\ &= G_i + P_i C_{i-1} \end{aligned}$$

- Block  $i : j$  *generates* a carry if the block produces a carry output ( $C_{i,out}$ ) independent of the block's carry input ( $C_{j,in}$ )
- Block  $i : j$  *propagates* a carry if the block produces a carry output ( $C_{i,out}$ ) whenever there is a carry input for the block ( $C_{j,in}$ )
- Example of a block with two bit slices

$$\begin{aligned} C_{i-1} &= G_{i-1} + P_{i-1} C_{i-2} \\ C_i &= G_i + P_i C_{i-1} \\ &= G_i + P_i (G_{i-1} + P_{i-1} C_{i-2}) \\ &= G_i + P_i G_{i-1} + P_i P_{i-1} C_{i-2} \\ &= (G_i + P_i G_{i-1}) + (P_i P_{i-1}) C_{i-2} \\ &= G_{i;j} + P_{i;j} C_{i-2} \end{aligned}$$

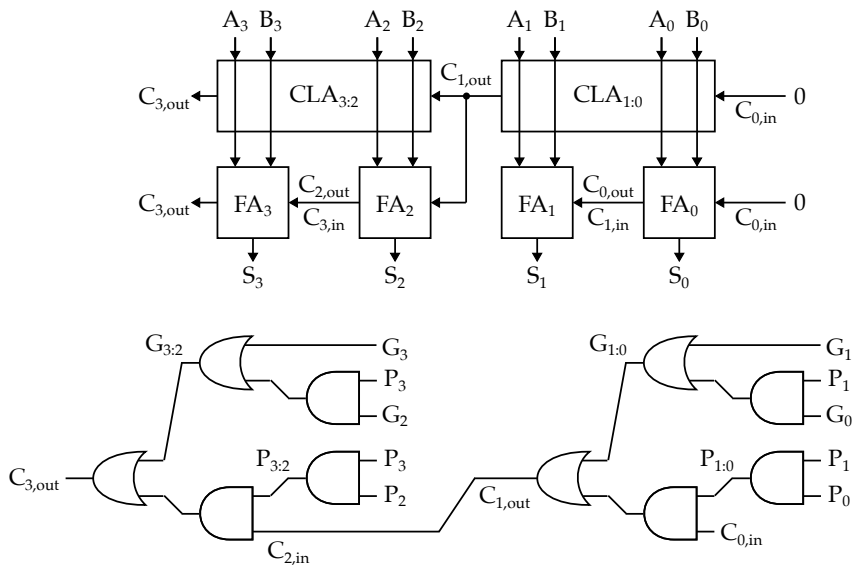- *Key Idea:* We can compute all of the generate and propagate signals without knowing the carry in; then once we know the carry in we can quickly calculate the carry out



Gate	$t_{pd}$	$t_{cd}$
NOT	$1\tau$	$1\tau$
AND2	$3\tau$	$3\tau$
OR2	$4\tau$	$4\tau$
XOR2	$7\tau$	$7\tau$


Path	Propagation Delay
$A_0 \rightarrow S_3$	
$B_0 \rightarrow S_3$	
$A_0 \rightarrow C_{3,out}$	
$B_0 \rightarrow C_{3,out}$	

## 6.5. Subtractors

$$\begin{array}{r}
 0001 \\
 - 0001 \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0011 \\
 - 0001 \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0010 \\
 - 0001 \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0100 \\
 - 0001 \\
 \hline
 \end{array}
 \quad
 \begin{array}{r}
 0100 \\
 - 0011 \\
 \hline
 \end{array}$$
 
## 6.6. Half and Full Subtractors


- *Half subtractor* subtracts two one-bit numbers



A	B	X <sub>out</sub>	D
0	0		
0	1		
1	0		
1	1		





 
- *Full subtractor* subtracts two one-bit numbers with borrow in



$X_{in}$	A	B	$X_{out}$	D
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

   
## 6.7. Ripple-Carry Subtractor

- Ripple-carry subtractor* chains full subtractors together




## 7. Multipliers



### 7.1. 1x1b Multiplier

 

$A$	$B$	$P$
0	0	
0	1	
1	0	
1	1	

 

### 7.2. 1x4b Multiplier

  

## 7.3. 4x4b Multiplier

