

# ECE 2300 Digital Logic and Computer Organization

## Topic 5: Number Systems

<http://www.csl.cornell.edu/courses/ece2300>

School of Electrical and Computer Engineering

Cornell University

revision: 2025-10-05-14-17

### List of Problems

|          |                                  |          |
|----------|----------------------------------|----------|
| <b>1</b> | <b>Recall</b>                    | <b>2</b> |
| 1.A      | Limits . . . . .                 | 2        |
| 1.B      | Conversion . . . . .             | 3        |
| <b>2</b> | <b>Subtraction!</b>              | <b>4</b> |
| 2.A      | Sign Magnitude . . . . .         | 4        |
| 2.B      | "Half" of the problem . . . . .  | 5        |
| 2.C      | A Transistor Schematic . . . . . | 6        |
| 2.D      | The "Full" Solution . . . . .    | 7        |
| 2.E      | Timing Analysis . . . . .        | 8        |
| 2.F      | Adding Subtractors? . . . . .    | 9        |
| 2.G      | An alternative? . . . . .        | 9        |
| 2.H      | Comparison . . . . .             | 10       |

**Problem 1. Recall**

In this problem, we'll talk about the features of different number systems.

**Part 1.A Limits**

How many different numbers *can* be represented with 4 bits? 8 bits?  $n$  bits?

What is the largest 16 bit *unsigned* binary number? How about 32 bits? How about  $n$  bits?

What is the *range* (in the format  $[a, b]$ ) of the following  $n$  bit binary number systems?

| System              | Range |
|---------------------|-------|
| Unsigned            |       |
| Sign<br>Magnitude   |       |
| Two's<br>Complement |       |

**Part 1.B Conversion**

Convert the following decimal numbers into each number system. **Represent each number with 6 bits.** If it is not possible to represent the decimal number in that system, please denote so with an  $\times$ .

| Number | Unsigned | Sign-magnitude | 2's Complement |
|--------|----------|----------------|----------------|
| 0      |          |                |                |
| 1      |          |                |                |
| -1     |          |                |                |
| 9      |          |                |                |
| 26     |          |                |                |
| 47     |          |                |                |
| -7     |          |                |                |
| -19    |          |                |                |

Convert the following *binary* numbers *from* each number system. **Assume each number has 6 bits.**

| Binary | Unsigned | Sign-magnitude | 2's Complement |
|--------|----------|----------------|----------------|
| 000000 |          |                |                |
| 000101 |          |                |                |
| 011010 |          |                |                |
| 001011 |          |                |                |
| 100000 |          |                |                |
| 111111 |          |                |                |
| 110101 |          |                |                |
| 101001 |          |                |                |

**Problem 2. Subtraction!**

In this problem, we consider *subtraction* and how to efficiently implement it for *unsigned* numbers.

**Part 2.A Sign Magnitude**


In the spirit of *regularity*, we may consider re-using our adder (from lecture) to do subtraction.

A perhaps naive approach to compute  $a - b$  would be to rewrite it as  $a + (-b)$ . Of course, with *unsigned* numbers, representing  $-b$  might be difficult. Instead, we turn to *Sign Magnitude* numbers.

This yields a simple “algorithm” of sorts. **Use the same, smallest possible bitwidth for  $a$  and  $b$ .** Prepend a bit to both  $a$  and  $b$  (that is, place it in the most significant position). Prepend a 0 to  $a$  and a 1 to  $b$  to negate it. Then, we use our fantastic adder implementations to add  $a$  and  $-b$ , yielding  $a - b$ .

But, does this work? **Let’s find out by trying a few examples.**

 Try to compute  $7 - 4$  and  $11 - 7$  with this method.



**Does this method work? Why or why not?**

---

---

---

**Part 2.B “Half” of the problem**

The disappointing results from *Signed Magnitude* motivates specialized hardware for subtraction.


In fact, we can implement a *subtractor* using a structure analogous to an adder. However, we abandon the notion of a *carry* for that of a *borrow*. Otherwise, the interface is almost *identical* (*modularity*).

A borrow means the current bit of  $a$  is not large enough, so we must “borrow” from the next bit.

A *Half Subtractor* subtracts two one-bit numbers  $a$  and  $b$ .

It produces the *difference*  $d = a - b$  and a *borrow* bit.

 **Complete the truth table for this building block.**



| A | B | X <sub>out</sub> | D |
|---|---|------------------|---|
| 0 | 0 |                  |   |
| 0 | 1 |                  |   |
| 1 | 0 |                  |   |
| 1 | 1 |                  |   |

*Hint: when you borrow, you are “using” the next bit ( $2 \times$  larger), so, in this case, what should D be?*


**Write the boolean expressions for D and X<sub>out</sub>.**

**Complete a gate-level implementation of a Half Subtractor.**

**Part 2.C A Transistor Schematic**


Let's consider the transistor schematic for  $X_{\text{out}}$  from our *Half Subtractor*.

 **Complete the transistor schematic for  $X_{\text{out}}$**



It's *likely* that your schematic uses 8 transistors. However, we can optimize this.

 
Your implementation *likely* uses a AND/OR and an inverter. But, it would be much more efficient if we used an NAND/NOR and an inverter. **Simplify the boolean expression to use a NAND/NOR and a *single inverter* and draw the new transistor schematic.**



*Hint: try negating your current expression twice, then use De Morgan's to simplify the expression.*

 **Part 2.D The “Full” Solution**


Let's extend our half subtractor into a *Full Subtractor* so that we can chain them together. We extend our previous interface to also include a borrow-in. **Complete the truth table for this building block.**



| A | B | $X_{in}$ | $X_{out}$ | D |
|---|---|----------|-----------|---|
| 0 | 0 | 0        |           |   |
| 0 | 0 | 1        |           |   |
| 0 | 1 | 0        |           |   |
| 0 | 1 | 1        |           |   |
| 1 | 0 | 0        |           |   |
| 1 | 0 | 1        |           |   |
| 1 | 1 | 0        |           |   |
| 1 | 1 | 1        |           |   |

Write the boolean expressions for D and  $X_{out}$ .


Complete a gate-level implementation of a Full Subtractor.

 



 **Part 2.F Adding Subtractors?**

We can put several *Full Subtractors* together to create a *Ripple Carry Subtractor*.



Using the timing analysis from before, what is the propagation delay through this network?

\_\_\_\_\_

Generally, if we have an  $n$ -bit Ripple-Carry, what is the propagation delay?

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

That's not so good... How can we make our subtractor faster?

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

**Part 2.G An alternative?**

Recall from lecture, that subtraction can be implemented with an adder in one of the number systems. Which number system was this?

\_\_\_\_\_

How do we use this number system to implement subtraction?

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

## Part 2.H Comparison

Compare both subtractor implementations (dedicated vs 2's complement). Is one definitely better than the other? Which would you use in an add/sub unit? Which better fits our course principles of modularity, hierarchy, and regularity?

This image shows a single sheet of white paper with horizontal ruling lines. The lines are evenly spaced and run across the width of the page. There are no margins, text, or other markings on the paper.

## Hints

Compare qualitative and/or quantitative area and timing (see T02 practice problems for a simple area model). For a  $n$  bit unsigned number, we must include a sign bit for 2's complement addition. Do our subtractor need this?

*Good luck for Prelim 1. You got this!*