


ECE 2300 Digital Logic and Computer Organization Fall 2024

Topic 6: Sequential Logic Gates

School of Electrical and Computer Engineering
Cornell University

revision: 2024-10-03-10-14

1	Latches, Flip-Flops, and Registers	3
1.1.	SR Latch	3
1.2.	D Latch	4
1.3.	D Flip-Flop	5
1.4.	D Flip-Flop with Reset	6
1.5.	D Flip-Flop with Reset and Enable	6
1.6.	Multi-Bit Register	7
2	Sequential Gate-Level Networks	8
3	Sequential Gate-Level Timing	10
3.1.	Setup Time Constraint	13
3.2.	Hold Time Constraint	18
3.3.	Summary of Sequential Gate-Level Timing	21

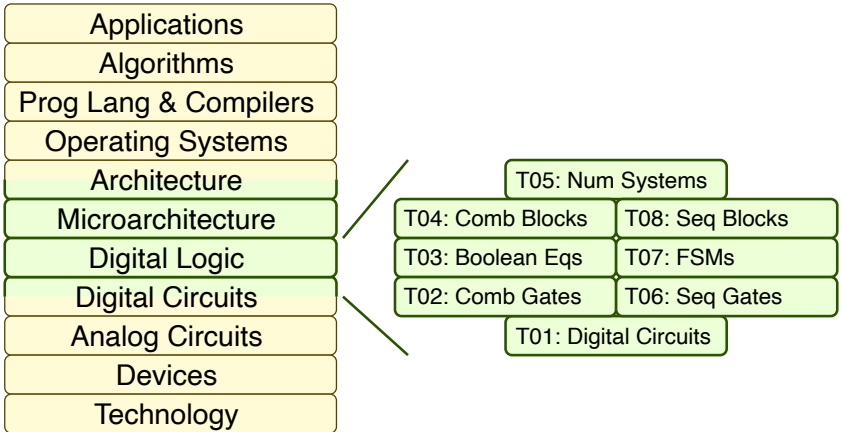


Copyright © 2024 Christopher Batten. All rights reserved. This handout was prepared by Prof. Christopher Batten at Cornell University for ECE 2300 / ENGRD 2300 Digital Logic and Computer Organization. Download and use of this handout is permitted for individual educational non-commercial purposes only. Redistribution either in part or in whole via both commercial or non-commercial means requires written permission.


1. Latches, Flip-Flops, and Registers

- *Combinational Logic*: outputs only depend on current inputs
- *Sequential Logic*: outputs depend on current inputs *and previous inputs*

1.1. SR Latch

 



S	R	X	Q
0	0		
0	1		
1	0		
1	1		

 


- *SR Latch*: bi-stable state element with set and reset inputs

  1.2. D Latch

- *SR Latch*: Asserting one input determines *what* the new state should be but also *when* it should change
- *D Latch*: One input controls *what* the next state should be, while second input controls *when* the state should change






clk	D	\bar{D}	S	R	X	Q
0	?					
1	0					
1	1					

 


   1.3. D Flip-Flop


- *D Latch*: Input is *sampled* continuously when clock is high
- *D Flip-Flop*: Input is only *sampled* at a specific instance in time (on the rising edge of the clock)




1.4. D Flip-Flop with Reset

 


1.5. D Flip-Flop with Reset and Enable

 


1.6. Multi-Bit Register

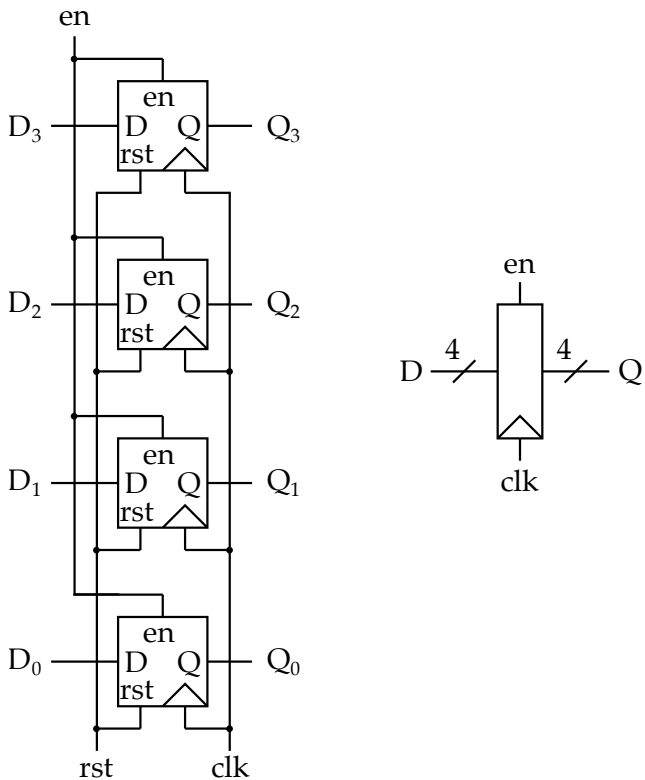

2. Sequential Gate-Level Networks

 


clk	A	B	X	Y	Z
0	0	0			
1	0	1			
0	0	1			
1	1	0			
0	1	0			
1	0	0			

 


- Convention for tables with implicit clock
 - One row per clock cycle
 - Inputs represent values before the rising edge
 - Other signals represent stable values after the rising edge

A	B	X	Y	Z
0	0			
0	1			
1	0			
0	0			

2. Sequential Gate-Level Networks

 


clk	A	B	C	V	W	X	Y	Z
0	0	0	0					
1	1	1	1					
0	1	1	1					
1	1	0	0					
0	1	0	0					
1	0	0	0					

 

3. Sequential Gate-Level Timing


- Critical Path for Combinational Gate-Level Networks:** longest propagation path delay from any input to any output

Gate	t_{pd}	t_{cd}
NOT	1τ	1τ
NAND2	2τ	1τ
NOR2	3τ	1τ
AND2	3τ	1τ
OR2	4τ	1τ

 

Path	Propagation Delay	Critical Path?
$a \rightarrow \text{NOT} \rightarrow \text{NAND2} \rightarrow \text{NOR2} \rightarrow y$		
$b \rightarrow \text{NAND2} \rightarrow \text{NOR2} \rightarrow y$		
$c \rightarrow \text{NOT} \rightarrow \text{NOR2} \rightarrow y$		

 - Identify all paths from any input to any output




Path

D → AND2 → NOR2 → NOR2 → AND2 → NOR2 → NOR2 → Q


Critical Path for Combinational Gate-Level Networks

 - Longest propagation path delay from:
 - any input to any output




Critical Path for Sequential Gate-Level Networks

 - Longest propagation path delay from:
 - any input to any output
 - any input to any flip-flop
 - any flip-flop to any flip-flop
 - any flip-flop to any output







3.1. Setup Time Constraint

 

Clock-to-Q Propagation Delay ($t_{pd,cq}$)


Setup Time (t_{setup})

  

  

Setup Time Constraint or Max-Delay Constraint

 Consider the following sequential gate-level network.




Highlight the critical path on the above gate-level network. Use the setup time constraint to derive an equation for the minimum clock period or cycle time (T_c) in terms of the following parameters.

- Flip-flop clock-to-Q propagation delay ($t_{pd,cq}$)
- Flip-flop setup time (t_{setup})
- Propagation delay of NOR2 ($t_{pd,nor2}$)
- Propagation delay of NAND2 ($t_{pd,nand2}$)



Calculate the minimum clock period or cycle time (T_c) given the delay model we have developed in this topic.



3.2. Hold Time Constraint

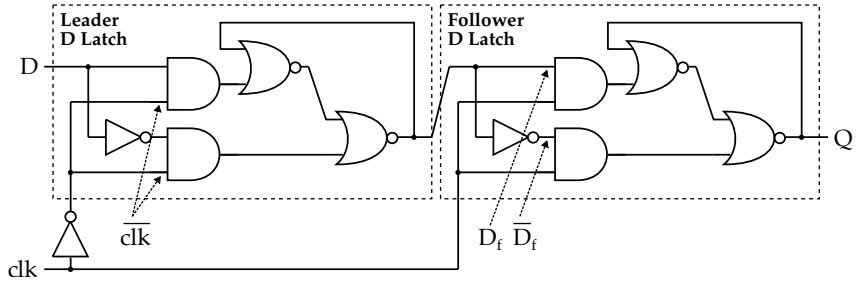

Clock-to-Q Contamination Delay ($t_{cd,cq}$)

Hold Time (t_{hold})

  

  

Hold Time Constraint or Min-Delay Constraint



3.3. Summary of Sequential Gate-Level Timing

