


ECE 2300 Digital Logic and Computer Organization Fall 2024

Topic 7: Finite State Machines

School of Electrical and Computer Engineering
Cornell University


revision: 2024-10-10-10-12

1	From Logic Gates to Finite-State Machines	3
2	Finite-State Machines	6
2.1.	Moore FSMs	7
2.2.	Mealy FSMs	8
2.3.	FSM State Encoding	9
2.4.	Designing FSMs	10
2.5.	Factoring FSMs	12
3	From Finite-State Machines to Logic Gates	16
4	Modeling Finite-State Machines with Verilog	19
4.1.	Gate-Level Modeling of FSMs	19
4.2.	RTL Modeling of FSMs	21

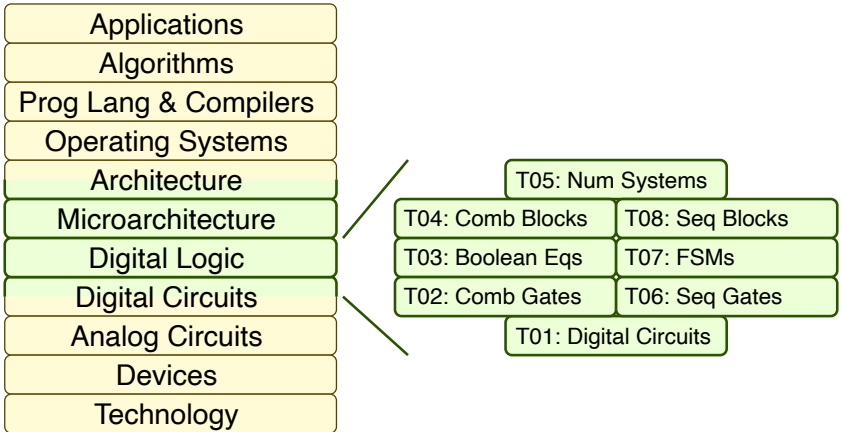

Copyright © 2024 Christopher Batten. All rights reserved. This handout was prepared by Prof. Christopher Batten at Cornell University for ECE 2300 / ENGRD 2300 Digital Logic and Computer Organization. Download and use of this handout is permitted for individual educational non-commercial purposes only. Redistribution either in part or in whole via both commercial or non-commercial means requires written permission.

 
1. From Logic Gates to Finite-State Machines



Assume all flip-flops are reset to zero.

S_0	$S_{0,next}$	Y
0		
1		

 
1. From Logic Gates to Finite-State Machines



Assume all flip-flops are reset to zero.

A	S_0	$S_{0,next}$	Y
0	0		
0	1		
1	0		
1	1		

 
1. From Logic Gates to Finite-State Machines



Assume all flip-flops are reset to zero.


S_1	S_0	$S_{1,next}$	$S_{0,next}$	Y
0	0			
0	1			
1	0			
1	1			

2. Finite-State Machines

 


- *Finite state machines* (FSM) are abstractions for sequential gate-level networks
 - Finite number of inputs (A)
 - Finite number of outputs (Y)
 - Finite number of states (S)
 - Designated reset state
 - FSM transition function ($S_{next}(S, A)$)
 - FSM output function ($Y(S)$ or $Y(S, A)$)
- Two kinds of FSMs
 - Moore FSMs: Outputs only depend on current state ($Y(S)$)
 - Mealy FSMs: Outputs depend on current state and inputs ($Y(S, A)$)
- FSMs can be represented using:
 - FSM transition and output functions
 - FSM transition and output tables
 - FSM diagrams

2.1. Moore FSMs

 


cycle	0	1	2	3	4	5	6	7	8	9	10
A	0	0	1	0	0	0	1	1	0	1	0
S	00										
S_{next}	01										
Y	0										

S_1	S_0	A	$S_{1,next}$	$S_{0,next}$	Y
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			

 

2.2. Mealy FSMs

 


cycle	0	1	2	3	4	5	6	7	8	9	10
A	0	0	1	0	0	0	1	1	0	1	0
S	00										
S_{next}	01										
Y	0										

S_1	S_0	A	$S_{1,next}$	$S_{0,next}$	Y
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			

 2.3. FSM State Encoding

- Often there is freedom in choosing how to encode the states
- Different encodings result in different FSM transition and output functions (and thus produce different gate-level implementations)
- Two common FSM encodings
 - *Binary encoding* uses a binary to encode each state
 - *One-hot encoding* uses a separate bit to encode each state



S_2	S_1	S_0	A	$S_{1,next}$	$S_{0,next}$	Y
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
1	0	0	0			
1	0	0	1			

2.4. Designing FSMs

- Step 1. Understand problem statement, determine inputs/outputs
- Step 2. Choose Moore vs. Mealy, identify states, create state diagram
- Step 3. Determine state encoding
- Step 4. Create FSM state transition and output tables
- Step 5. Determine FSM state transition and output functions

Design an FSM with one input (A) and two outputs (Y, Z) which monitors the input and sets Y to one when it has seen two or more consecutive ones and sets Z to one when it has seen three or more consecutive ones.


Step 1. Understand problem statement, determine inputs/outputs

Step 2. Choose Moore vs. Mealy, identify states, create state diagram


Step 3. Determine state encoding**Step 4. Create FSM state transition and output tables****Step 3. Determine FSM state transition and output functions**

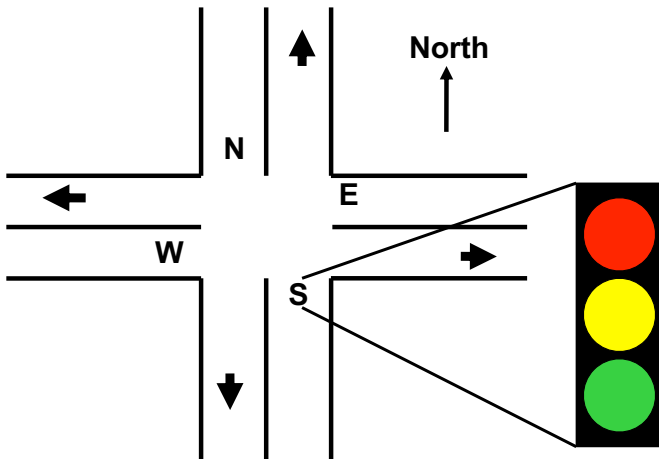2.5. Factoring FSMs


- Design a FSM for a traffic light controller
- Four-way intersection with traffic lights
- Opposing lanes sequence together
 - Turn on green light for 20 seconds
 - Turn on yellow light for yellow 5 seconds
 - Turn on red light for 25 seconds
- Four scenarios
 - E/W green and N/S red for 20 seconds
 - E/W yellow and N/S red for 5 seconds
 - E/W red and N/S green for 20 seconds
 - E/W red and N/S yellow for 20 seconds




- Requires an FSM with 10 states
 - E/W green and N/S red1 for 5 seconds
 - E/W green and N/S red2 for 5 seconds
 - E/W green and N/S red3 for 5 seconds
 - E/W green and N/S red4 for 5 seconds
 - E/W yellow and N/S red for 5 seconds
 - E/W red and N/S green1 for 5 seconds
 - E/W red and N/S green2 for 5 seconds
 - E/W red and N/S green3 for 5 seconds
 - E/W red and N/S green4 for 5 seconds
 - E/W red and N/S yellow for 5 seconds

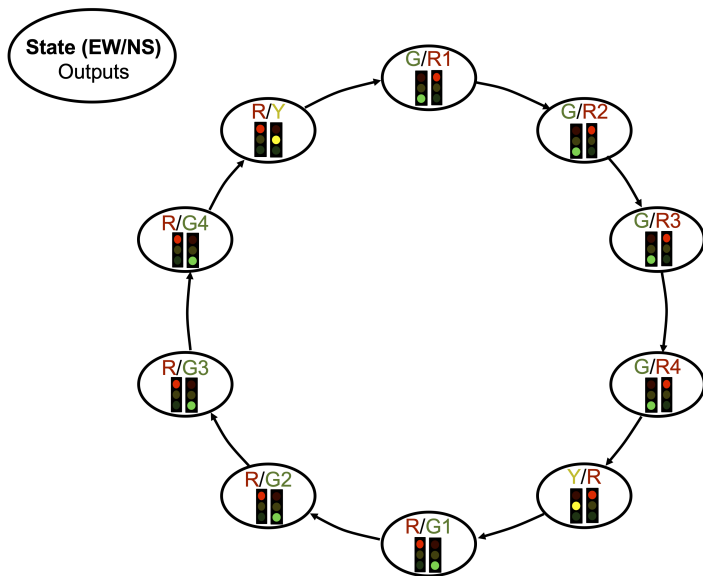

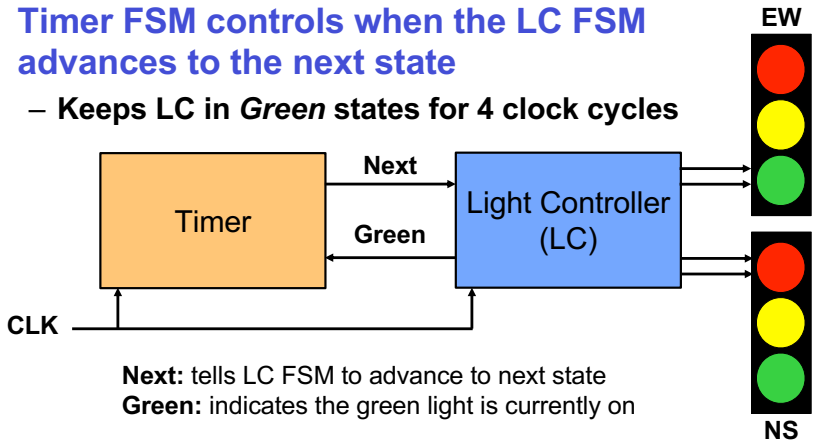
- Factoring FSMs involves breaking an FSM into multiple communicating FSMs
 - Simplifies large FSMs
 - May result in fewer states
- **Light Controller (LC) FSM has 4 states**
 - **G/R, Y/R, R/G, R/Y**
- **Timer FSM controls when the LC FSM advances to the next state**
 - **Keeps LC in Green states for 4 clock cycles**




Light Controller (LC) FSM

 

Timer FSM

 

 
3. From Finite-State Machines to Logic Gates



$$S_{1,next} = \bar{S}_1 S_0 A$$

$$S_{0,next} = \bar{S}_1 \bar{A} + \bar{S}_0 \bar{A}$$


$$Y = S_1 \bar{S}_0$$

 


$$S_{1,next} = \overline{S_1}S_0A$$

$$S_{0,next} = \overline{S_1}\overline{A} + \overline{S_0}\overline{A}$$

$$Y = \overline{S_1}S_0A$$

 

 Implement the following FSM at the gate level.



What does this FSM do?

S_1	S_0	A	$S_{1,next}$	$S_{0,next}$	Y
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

A	S_1S_0	00	01	11	10
0					
1					

A	S_1S_0	00	01	11	10
0					
1					

A	S_1S_0	00	01	11	10
0					
1					


4. Modeling Finite-State Machines with Verilog

4.1. Gate-Level Modeling of FSMs

```

1 module Detect01_GL
2 (
3   wire clk,
4   wire rst,
5   wire a
6 );
7 // Sequential: state flip-flops
8
9 wire s0, s0_next;
10
11 DFFR_GL s0_dffr
12 (
13   .clk (clk),
14   .rst (rst),
15   .q   (s0_next),
16   .d   (s0)
17 );
18
19 wire s1, s1_next;
20
21 DFFR_GL s1_dffr
22 (
23   .clk (clk),
24   .rst (rst),
25   .q   (s1_next),
26   .d   (s1)
27 );
28
29 // Combinational: state transition
30
31 assign s0_next = ( ~s1 & ~a ) | ( ~s0 & ~a );
32 assign s1_next = ~s1 & s0 & a;
33
34 // Combinational: output logic
35
36 assign y = s1 & ~s0;
37
38 endmodule


```

 

$$S_{1,next} = \bar{S}_1 S_0 A$$

$$S_{0,next} = \bar{S}_1 \bar{A} + \bar{S}_0 \bar{A}$$

$$Y = S_1 \bar{S}_0$$

 


Implement 00/11 detector in Verilog using gate-level modeling.

```

1 module Detect00or11_GL
2 (
3   wire clk,
4   wire rst,
5   wire a
6 );
7   // Sequential: state flip-flops
8
9   wire s0, s0_next;
10  DFFR_GL s0_dffr( .clk(clk), .rst(rst), .q(s0_next), .d (s0) );
11
12  wire s1, s1_next;
13  DFFR_GL s1_dffr( .clk(clk), .rst(rst), .q(s1_next), .d (s1) );

```

 

```

1 endmodule


```

4.2. RTL Modeling of FSMs

```

1 module Detect01_RTL
2 (
3   logic clk,
4   logic rst,
5   logic a
6 );
7   // Sequential: state register
8
9   localparam STATE_S0 = 2'b00;
10  localparam STATE_S1 = 2'b01;
11  localparam STATE_S2 = 2'b10;
12
13  logic state, state_next;
14
15  Register_2b_RTL state_reg
16  (
17    .clk (clk),
18    .rst (rst),
19    .q   (state_next),
20    .d   (state)
21  );
22
23  // Combinational: state transition
24  always_comb begin
25    case ( state )
26      STATE_S0 : state_next = ( a ) ? STATE_S0 : STATE_S1;
27      STATE_S1 : state_next = ( a ) ? STATE_S2 : STATE_S1;
28      STATE_S2 : state_next = ( a ) ? STATE_S1 : STATE_S0;
29    endcase
30  end
31
32  // Combinational: output
33  always_comb begin
34    case ( state )
35      STATE_S0 : y = 0;
36      STATE_S1 : y = 0;
37      STATE_S2 : y = 1;
38    endcase
39  end
40
41 endmodule


```

 

$$S_{1,next} = \bar{S}_1 S_0 A$$

$$S_{0,next} = \bar{S}_1 \bar{A} + \bar{S}_0 \bar{A}$$

$$Y = S_1 \bar{S}_0$$

 


Implement 00/11 detector in Verilog using RTL modeling.

```

1 module Detect00or11_RTL
2 (
3   logic clk, logic rst, logic a
4 );
5   // Sequential: state register
6   localparam STATE_S0 = 2'b00;
7   localparam STATE_S1 = 2'b01;
8   localparam STATE_S2 = 2'b10;
9   localparam STATE_S3 = 2'b11;
10  logic state, state_next;
11  Register_2b_RTL state_reg( .clk(clk), .rst(rst),
12                             .q(state_next), .d(state) );

```

 

```

1 endmodule

```