
 
 
 


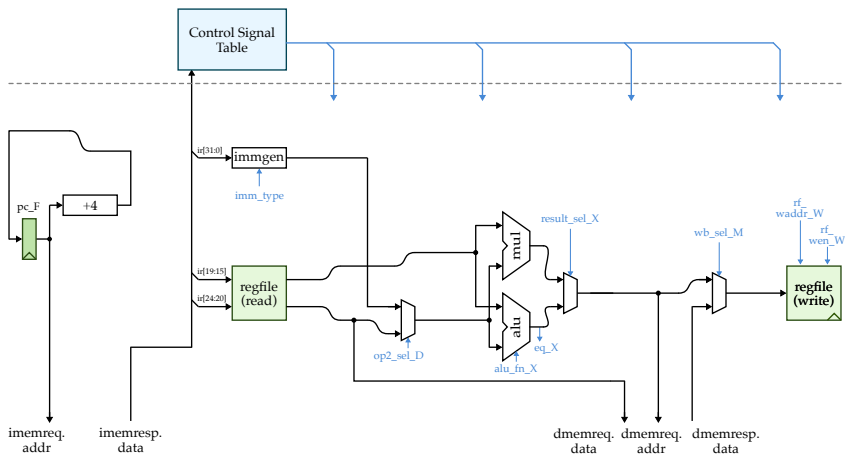3. Five-Stage Pipelined Processor

- Incrementally develop an unpipelined datapath
- Start with just arithmetic and memory instructions
- Keep data flowing from left to right
- Position control signal table early in the diagram
- Divide datapath/control into stages by inserting pipeline registers
- Keep the pipeline stages roughly balanced
- Forward arrows should avoid “skipping” pipeline registers



Pipeline diagrams


addi x1, x2, 1													
addi x3, x4, 1													
addi x5, x6, 1													

What would be the total execution time if these three instructions were repeated 10 times?



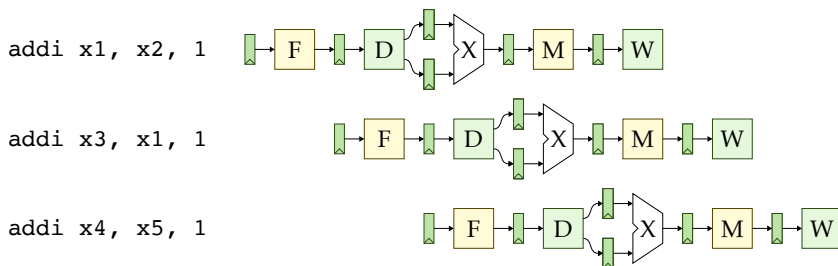3.1. RAW Data Hazards Through Registers

RAW data hazards occur when one instruction depends on a data value produced by a preceding instruction still in the pipeline.



addi x1, x2, 1													
addi x3, x1, 1													
addi x4, x5, 1													

Deriving the stall signal

```
stall_waddr_X_rs1_D =
    val_D && rs1_en_D && val_X && rf_wen_X
    && (inst_rs1_D == rf_waddr_X) && (rf_waddr_X != 0)
```

```
stall_waddr_M_rs1_D =
    val_D && rs1_en_D && val_M && rf_wen_M
    && (inst_rs1_D == rf_waddr_M) && (rf_waddr_M != 0)
```

```
stall_waddr_W_rs1_D =
    val_D && rs1_en_D && val_W && rf_wen_W
    && (inst_rs1_D == rf_waddr_W) && (rf_waddr_W != 0)
```

... similar for stall signals for rs2 source register ...

```
stall_D = val_D
    && (    stall_waddr_X_rs1_D || stall_waddr_X_rs2_D
          || stall_waddr_M_rs1_D || stall_waddr_M_rs2_D
          || stall_waddr_W_rs1_D || stall_waddr_W_rs2_D )
```

```
stall_F = stall_D
```


Draw the pipeline diagram assuming data hazards are resolved with hardware stalling

addi x1, x0, 100													
addi x2, x0, 4													
add x3, x1, x2													
addi x0, x0, 0													
addi x4, x3, 3													

Deriving the bypass and stall signals

```
stall_waddr_X_rs1_D = 0
bypass_waddr_X_rs1_D =
    val_D && rs1_en_D && val_X && rf_wen_X
    && (inst rs1 D == rf_waddr X) && (rf_waddr X != 0)
```

Pipeline diagram showing multiple hardware bypass paths

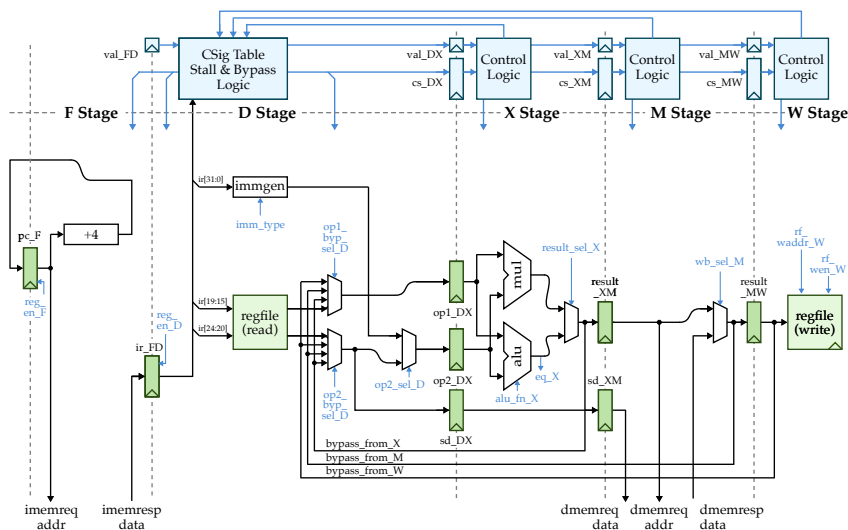[illegible]

Handling load-use RAW dependencies

ALU-use latency is only one cycle, but load-use latency is two cycles.

[illegible][illegible]

```

stall_load_use_X_rs1_D =
    val_D && rs1_en_D && val_X && rf_wen_X
    && (inst_rs1_D == rf_waddr_X) && (rf_waddr_X != 0)
    && (op_X == lw)

stall_load_use_X_rs2_D =
    val_D && rs2_en_D && val_X && rf_wen_X
    && (inst_rs2_D == rf_waddr_X) && (rf_waddr_X != 0)
    && (op_X == lw)

stall_D =
    val_D && ( stall_load_use_X_rs1_D || stall_load_use_X_rs2_D )

bypass_waddr_X_rs1_D =
    val_D && rs1_en_D && val_X && rf_wen_X
    && (inst_rs1_D == rf_waddr_X) && (rf_waddr_X != 0)
    && (op_X != lw)

bypass_waddr_X_rs2_D =
    val_D && rs2_en_D && val_X && rf_wen_X
    && (inst_rs2_D == rf_waddr_X) && (rf_waddr_X != 0)
    && (op_X != lw)

```

Pipeline diagram for simple assembly sequence

Draw a pipeline diagram illustrating how the following assembly sequence would execute on a fully bypassed pipelined TinyRV1 processor. Include microarchitectural dependency arrows to illustrate how data is transferred along various bypass paths.

[illegible]

3.4. RAW Data Hazards Through Memory

So far we have only studied RAW data hazards through registers, but we must also carefully consider RAW data hazards through memory.

SW x1, 0(x2)

```
lw x3, 0(x4) # RAW dependency occurs if R[x2] == R[x4]
```

[illegible]