

ECE 5745 Complex Digital ASIC Design


Topic 3: CMOS Circuits

Christopher Batten


School of Electrical and Computer Engineering
Cornell University

<http://www.csl.cornell.edu/courses/ece5745>

Part 1: ASIC Design Overview

 

Topic 1
Hardware
Description
Languages


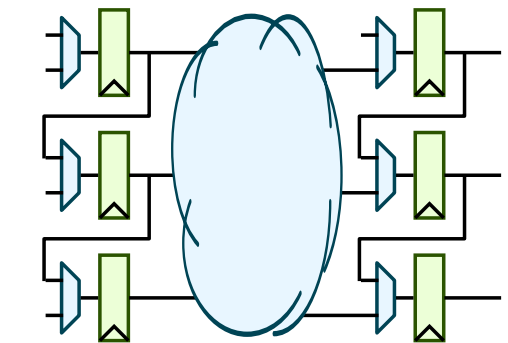


Topic 8
Testing and Verification


Topic 4
Full-Custom
Design
Methodology

Topic 6
Closing
the
Gap


Topic 5
Automated
Design
Methodologies

  

Topic 3
CMOS Circuits

 


Topic 7
Clocking, Power Distribution,
Packaging, and I/O

 


Topic 2
CMOS Devices


CMOS Logic, State, Interconnect

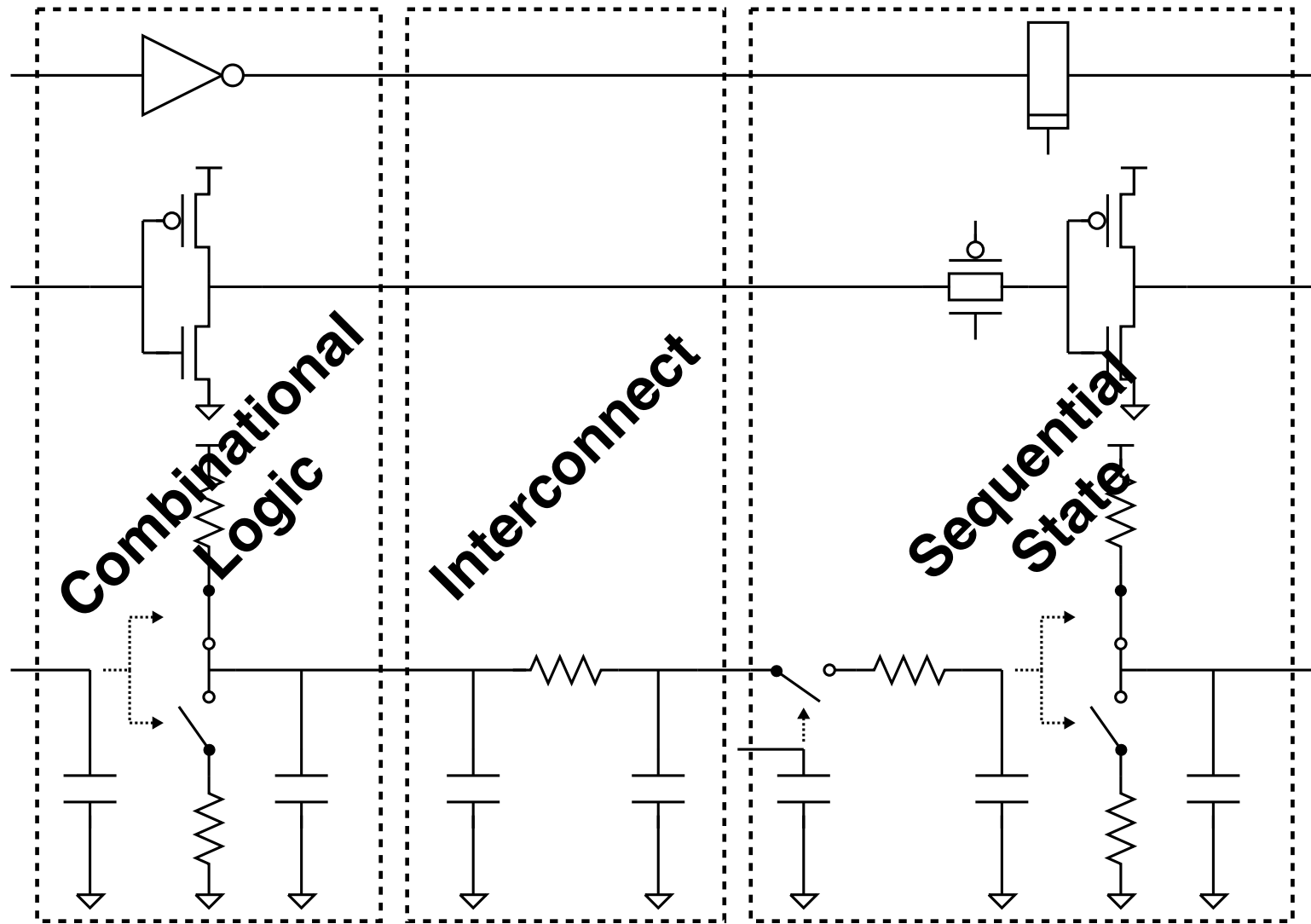



CMOS Logic, State, Interconnect

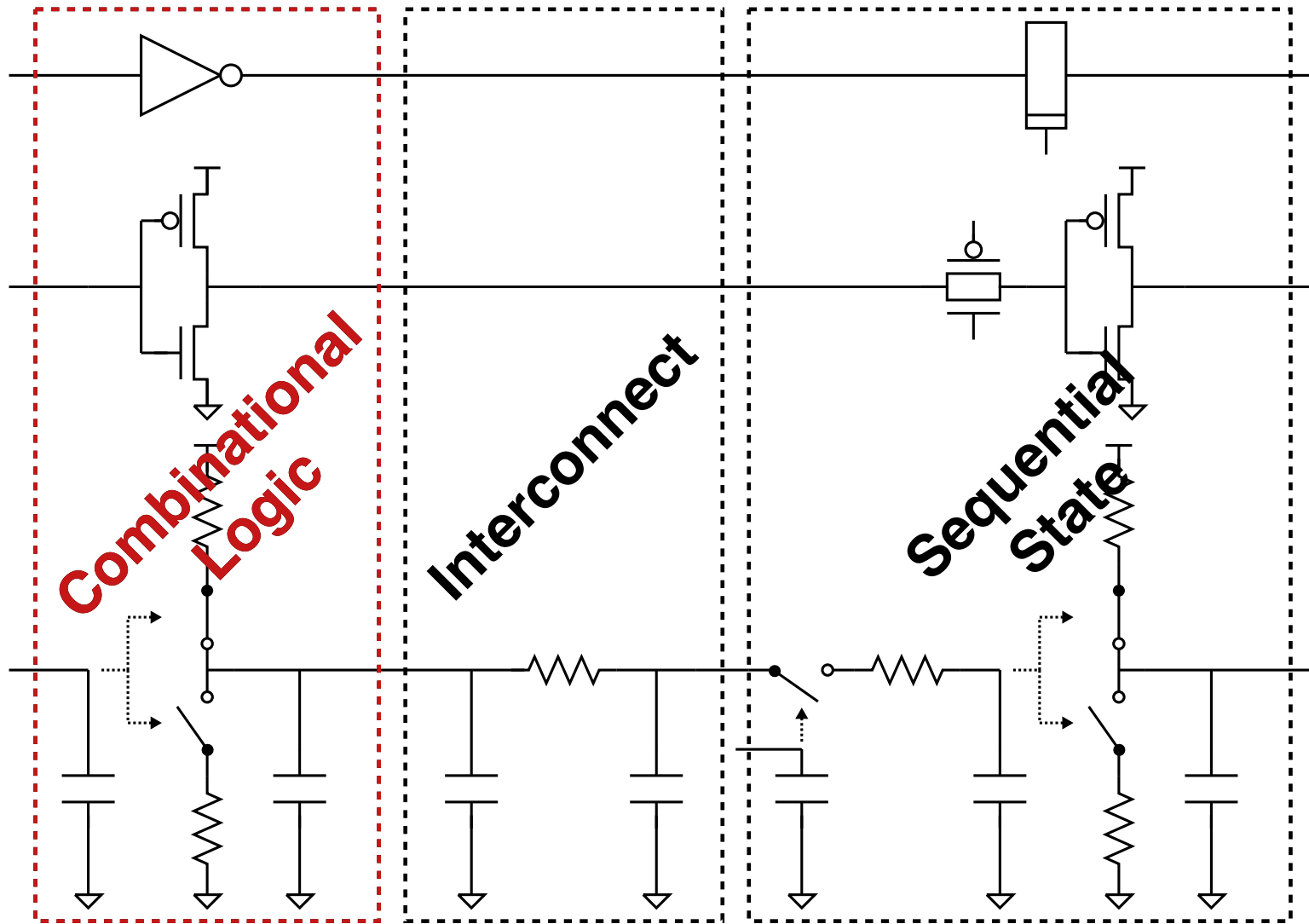

CMOS Inverter Simple RC Model

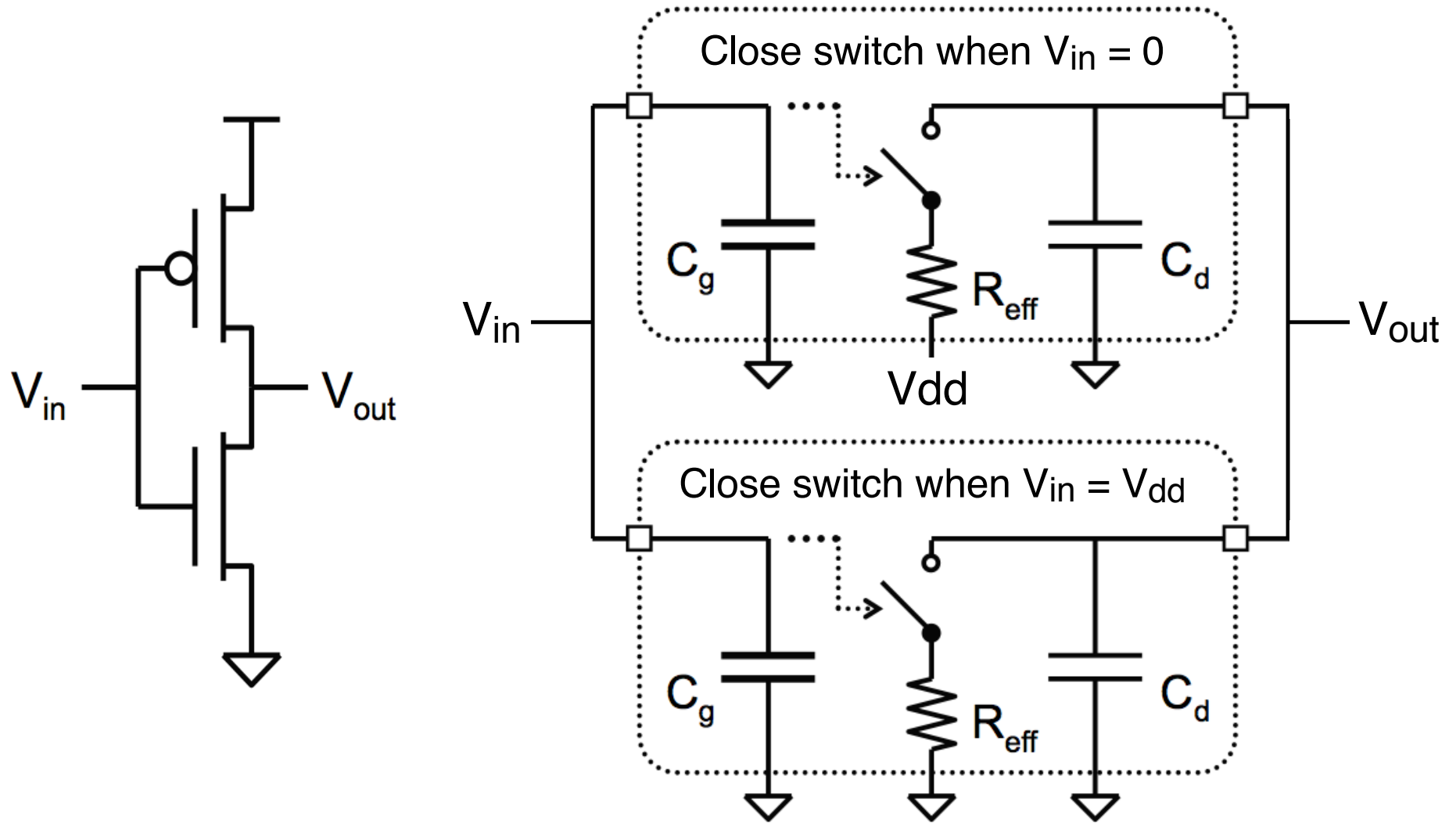

CMOS Inverter Simple RC Model

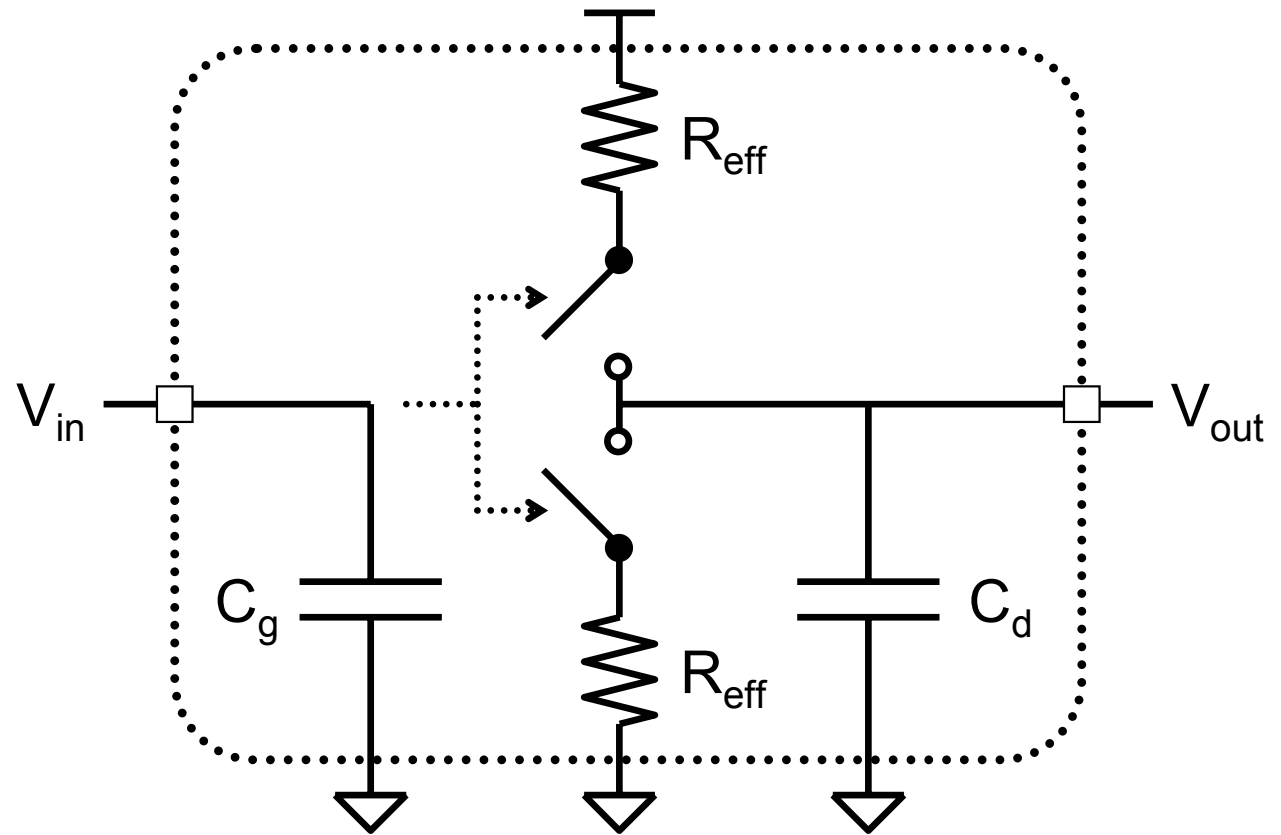 


$$R_{eff} = R_{eff,N} = R_{eff,P}$$


$$C_g = C_{g,N} + C_{g,P}$$

$$C_d = C_{d,N} + C_{d,P}$$

CMOS Inverter Layout

 


CMOS Inverter

 

Let's make the following assumptions



1. All transistors are minimum length
2. All gates should have equal rise/fall times. Since PMOS are twice as slow as NMOS they must be twice as wide to have the same effective resistance
3. Normalize all transistor widths to minimum width NMOS

Series Transistors

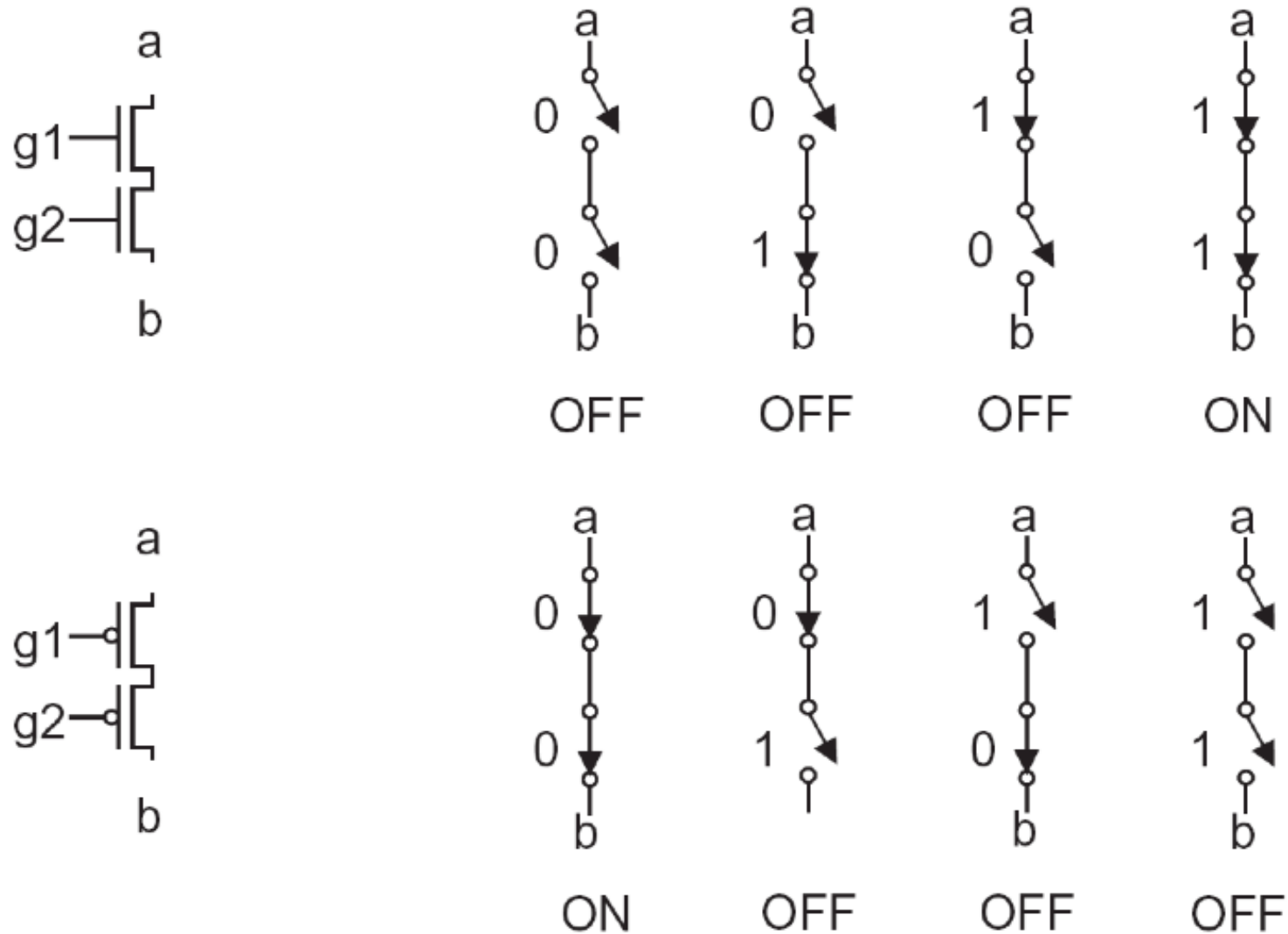


Adapted from [Weste'11]


Parallel Transistors

  


OFF

 



ON

 


ON

 


ON

  


ON

 

ON

 


ON

 


OFF

Adapted from [Weste'11]

 
Series/Parallel Transistor Networks are Natural Duals




Conducts if $A=0$

 


Conducts if $A=0$ **OR** $B=0$

 


Conducts if $A=0$ **AND** $B=0$

 

Conducts if $A=1$

 


Conducts if $A=1$ **AND** $B=1$

 

Conducts if $A=1$ **OR** $B=1$

CMOS Static Logic Style


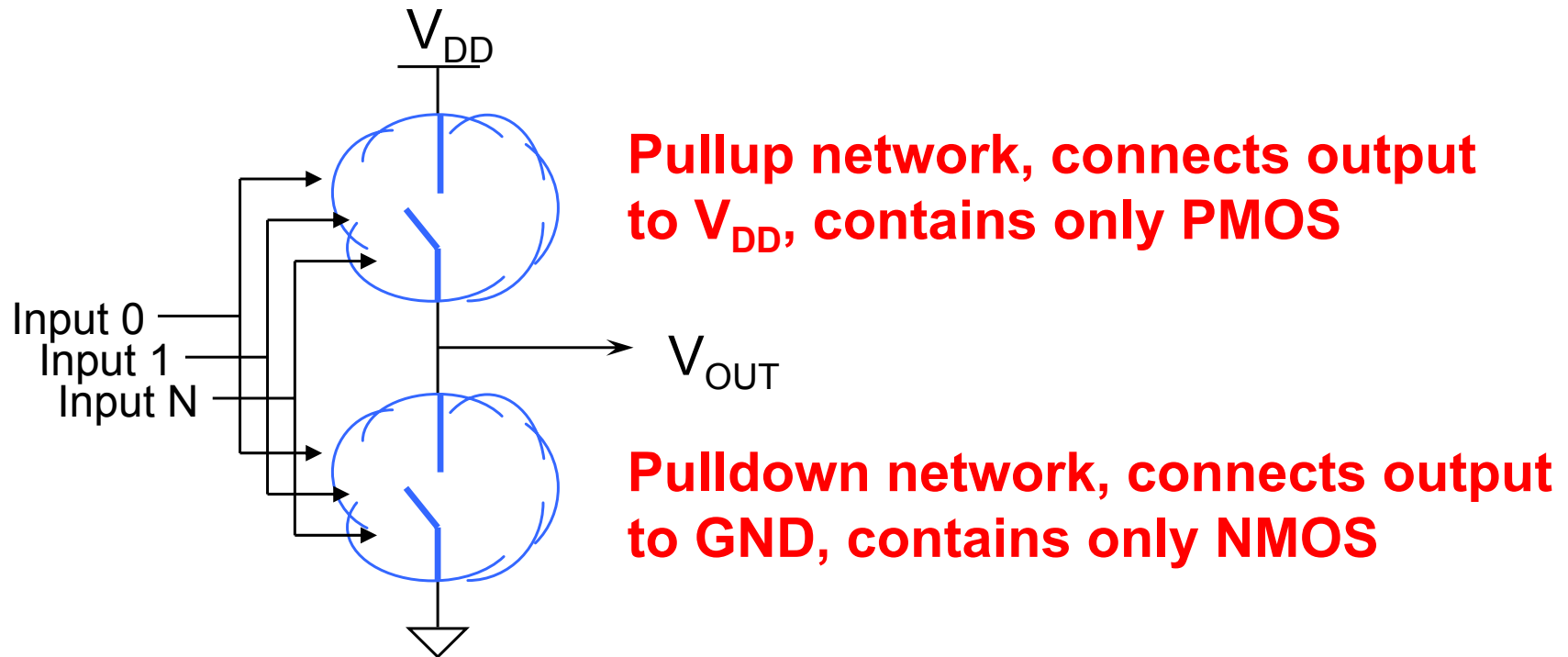


For every set of input logic values, either pullup or pulldown network makes connection to VDD or GND



- If both connected, power rails would be shorted together
- If neither connected, output would float (tristate logic)

NAND/NOR Static CMOS Logic Gates

NAND Gate

  


NOR Gate

  

Approach for Designing More Complex Gates

- ▶ Goal is to create a logic function $f(x_1, x_2, \dots)$
 - ▷ We can only implement inverting logic with one CMOS stage
- ▶ Implement pulldown network
 - ▷ Write $PD = \overline{f(x_1, x_2, \dots)}$
 - ▷ Use parallel NMOS for OR of inputs
 - ▷ Use series NMOS for AND of inputs
- ▶ Implement pullup network
 - ▷ Write $PU = f(x_1, x_2, \dots) = g(\overline{x_1}, \overline{x_2}, \dots)$
 - ▷ Use parallel PMOS for OR of inverted inputs
 - ▷ Use series PMOS for AND of inverted inputs

Complex Logic Gate Example



 


$$f = \overline{(A + B) \cdot C}$$

$$PD = (A + B) \cdot C$$


$$\begin{aligned} PU &= \overline{(A + B) \cdot C} \\ &= \overline{(A + B)} + \overline{C} \\ &= (\overline{A} \cdot \overline{B}) + \overline{C} \end{aligned}$$

   Single- vs. Multi-Stage Static CMOS Logic



Adapted from [Weste'11]


Multiple Stages of Static CMOS Logic

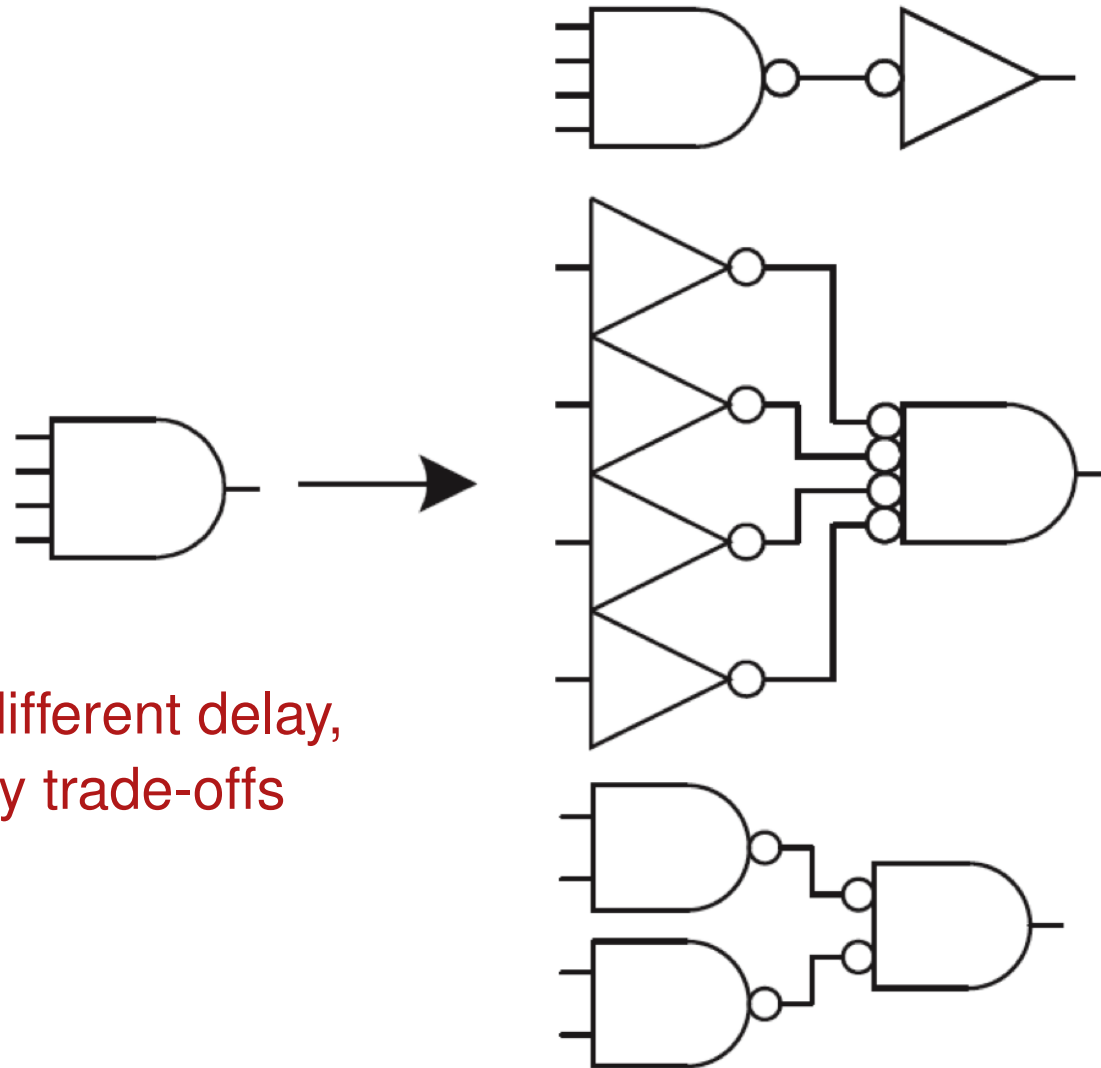

Each design has different delay,
area, and energy trade-offs


Adapted from [Weste'11]

CMOS Pass-Transistor Logic Style

 

Adapted from [Weste'11]

CMOS Transmission Gate Multiplexer

 

$g = 0, gb = 1$




$g = 1, gb = 0$






Input

Output

$g = 1, gb = 0$





 


$g = 1, gb = 0$

   



Adapted from [Weste'11]

CMOS Tri-State Buffers

     




Adapted from [Weste'11]

Various Multiplexer Implementations

  


Each design has different delay, area, and energy trade-offs

   Simple first-order analysis can help suggest some of these trade-offs




Adapted from [Weste'11]

Larger Tri-State Multiplexers






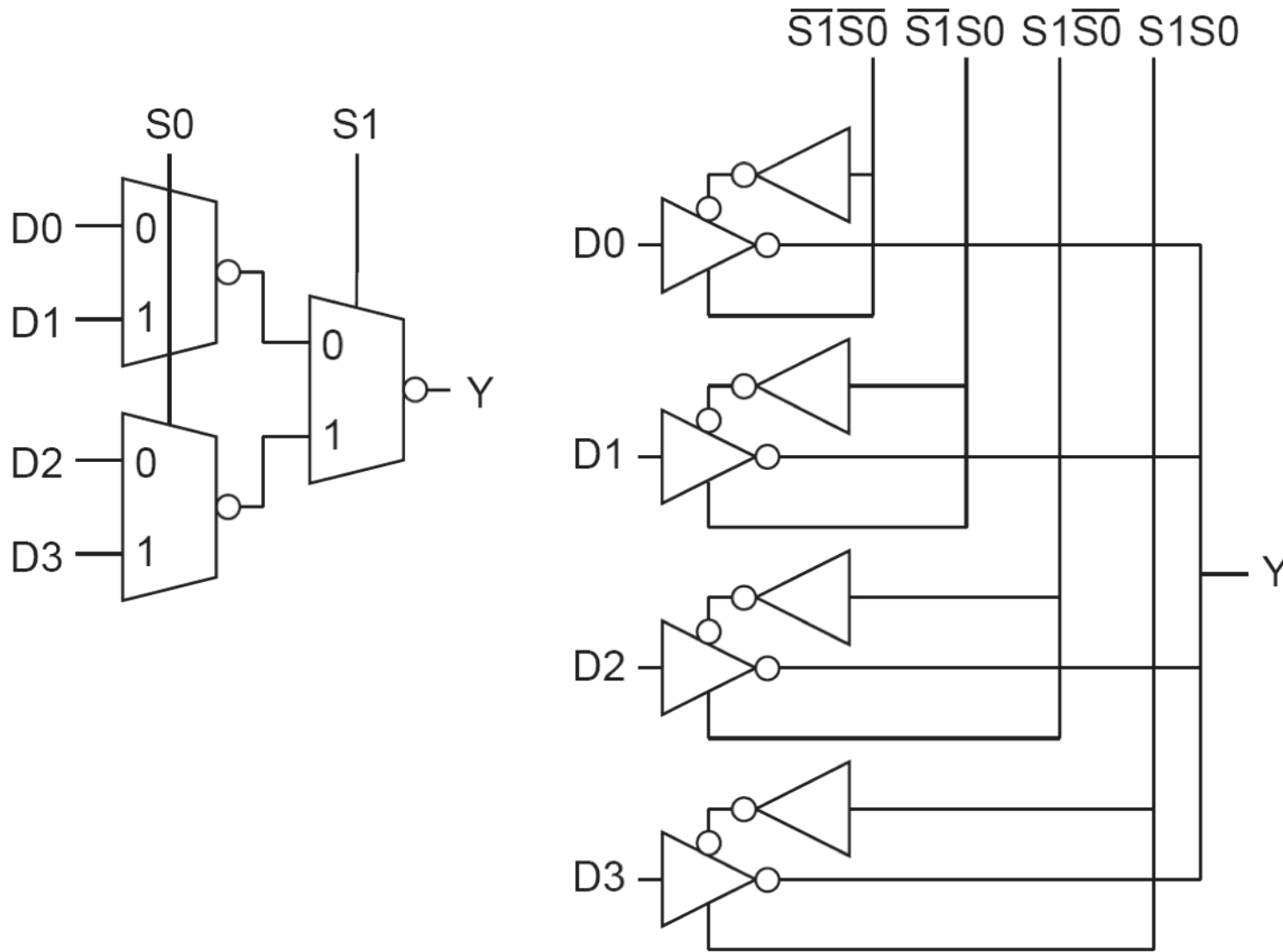


Adapted from [Weste'11]

CMOS Logic, State, Interconnect




 


Level-High Latch

      



Adapted from [Weste'11]

Positive-Edge Triggered Flip-Flop

    

Adapted from [Weste'11]

Positive-Edge Triggered Flip-Flop

 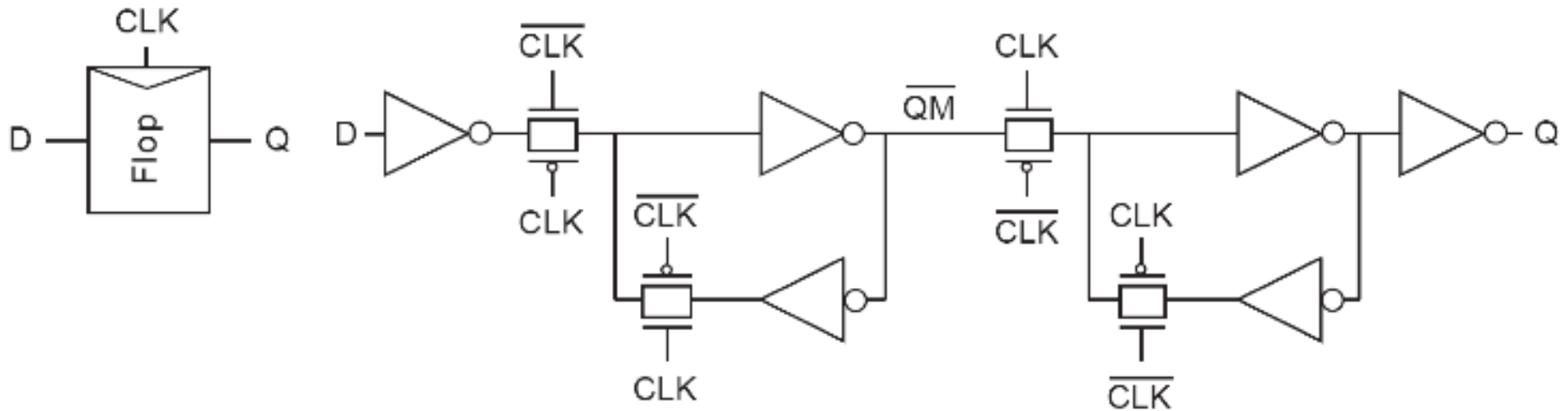

Adapted from [Weste'11]

Take-Away Points

- ▶ We have reviewed basic CMOS circuit implementations
 - ▷ Combinational Logic: static CMOS, pass-transistor, tri-state buffers
 - ▷ Sequential State: latches, flip-flops
- ▶ In the next two sections, we will explore various methodologies which enable mapping designs written in a hardware-description language down into these circuits
- ▶ In the next part of the course, we will explore the details of how to quantitatively evaluate the cycle time, area, and energy of these circuits

Acknowledgments

- ▶ [Weste'11] N. Weste and D. Harris, "CMOS VLSI Design: A Circuits and Systems Perspective," 4th ed, Addison Wesley, 2011.